

Magnetic Circuits

$$H \cdot l = NI$$

↓
magnetic field ↓ mean path length

SI unit of magnetic field: A/m

$$B = \mu_0 \mu_r H$$

↑ flux density ↓ flux

$$B = \frac{\mu_0 \mu_r N I}{l}$$

$$\Phi = B \times A$$

↓
T m² (Wb)
SI unit

$$\lambda = N\Phi$$

↓ flux linkage

$$L = \lambda/I$$

↓ inductance

H → magnetic field outside

B → magnetic field inside

$$\Phi = \frac{NI\mu_0\mu_r A}{l} \Rightarrow \Phi = \frac{NI}{(l/\mu_0\mu_r A)} \rightarrow \text{magneto motive force}$$

(l/\mu_0\mu_r A) → reluctance

EMF ⇔ mmf, Resistance ⇔ Reluctance, I ⇔ Φ

Q: A magnetic circuit has $A_c = 4 \times 4 \text{ cm}^2$, path length = 40cm and number of turns = 600. Taking $\mu_r = 6000$ for iron, calculate the exciting current for $B = 1.2 \text{ T}$. Calculate flux and inductance.


$$A = 16 \times 10^{-4} \text{ m}^2, l = 40 \times 10^{-2} \text{ m}, N = 600$$

$$\Phi = BA = 1.2 \times 16 \times 10^{-4} = 19.2 \times 10^{-4} \text{ T m}^2$$

$$B = \frac{\mu_0 \mu_r N I}{l} \Rightarrow \frac{1.2 \times 40 \times 10^{-4}}{4\pi \times 10^{-7} \times 6 \times 10^3 \times 6 \times 10^2} = I$$

$$\therefore I = 1.05 \text{ A}$$
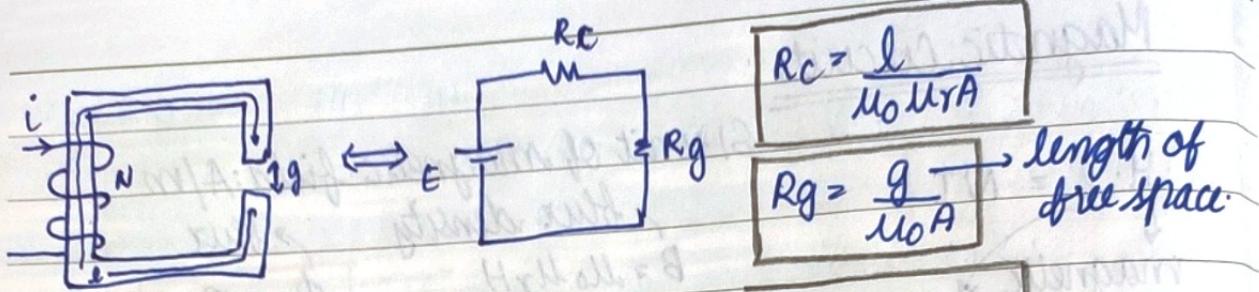
$$L = \frac{N\Phi}{I} = \frac{600 \times 19.2 \times 10^{-4}}{1.05} = 1.091 \text{ H}$$




$$i = E / (R_C + R_g) \Leftrightarrow \phi = \frac{NI}{\left(\frac{l}{\mu_0 \mu_r A} + \frac{g}{\mu_0 A} \right)} \Rightarrow \phi = \frac{NIA\mu_0}{\left(\frac{l}{\mu_r} + g \right)}$$

Q: A magnetic circuit has $A_c = 4 \times 4 \text{ cm}^2$, path length = 40cm and no. of turns = 600. Taking $\mu_r = 6000$ for iron and an air gap of 6mm, calculate inductance.

$$L = \frac{N\phi}{I} = \frac{N^2 I A \mu_0}{\left(\frac{l}{\mu_r} + g \right) I} = \frac{N^2 A \mu_0}{\left(\frac{l}{\mu_r} + g \right)} = \frac{600 \times 600 \times 16 \times 10^{-4} \times 4 \pi \times 10^{-7}}{\left(\frac{0.4}{6 \times 10^{-3}} + 6 \times 10^{-3} \right)}$$


$$= \frac{36 \times 16 \times 4 \times 3.14 \times 10^{-4}}{6.06} = \underline{\underline{0.1193 \text{ H}}}$$

Parallel magnetic circuit

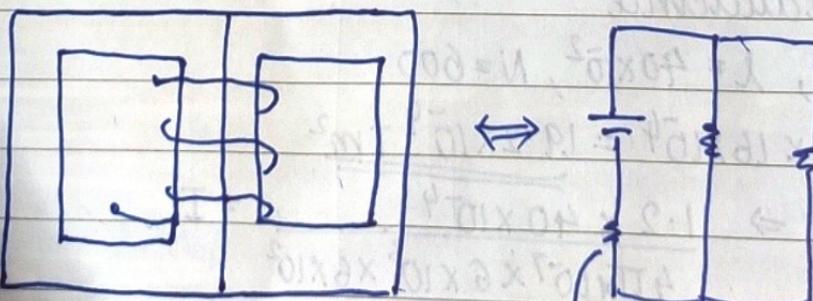

cancel out if area of cross section of both parts are equal.

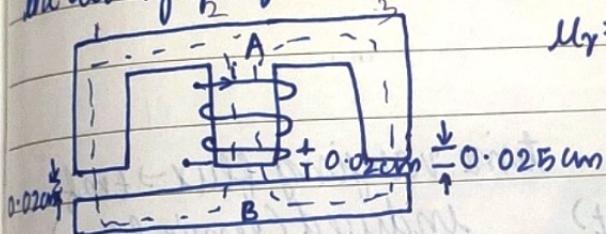(ii) For the magnetic core shown below, take $\mu_r = \infty$
 Mean length from A-B through outer limb = 0.5 m
 Mean length from A-B through inner limb = 0.2 m
 Area of CS of central limb = 2cm^2 , Area of CS of outer
 limb = 1cm^2 . It required to establish a flux of 0.75mWb in
 the air gap of central limb. Determine mmf of exciting coil.



$$\mu_r = \infty, R_{\text{material}} = 0$$

Only consider reluctance of
air gap

$$R_1 = g_L = \frac{2 \times 10^{-4}}{\mu_0 \times 1 \times 10^{-4}} = \frac{2}{\mu_0} \quad R_3 = \frac{2.5 \times 10^{-4}}{\mu_0 \times 1 \times 10^{-4}} = \frac{2.5}{\mu_0}$$


$$R_2 = \frac{2 \times 10^{-4}}{\mu_0 \times 2 \times 10^{-4}} = \frac{1}{\mu_0} \quad \text{equivalent:}$$

$$R_{\text{eq}} = R_2 + R_1 // R_3 = \frac{1}{\mu_0} + \frac{2}{\mu_0} \frac{2.5}{\mu_0} = \frac{4.5}{\mu_0}$$

$$R_{\text{eq}} = \frac{19}{9\mu_0}, \text{ mmf}(NI) = \phi \times R_{\text{eq}} \\ = \frac{0.75 \times 10^{-3} \times 19}{4\pi \times 10^{-7} \times 9} = \underline{\underline{1.26 \times 10^3 \text{A}}}$$

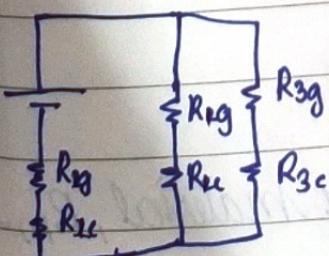(i) When $\mu_r = 5000$


Same procedure but $R_{\text{material}} \neq 0$



$$R_{\text{eq}} = R_g // R_3 + R_2 \\ = R_{cg} + R_{oc} + (R_{icg} + R_{ioc}) // (R_{3cg} + R_{3oc})$$

Paperkraft

DC Magnetization Curve

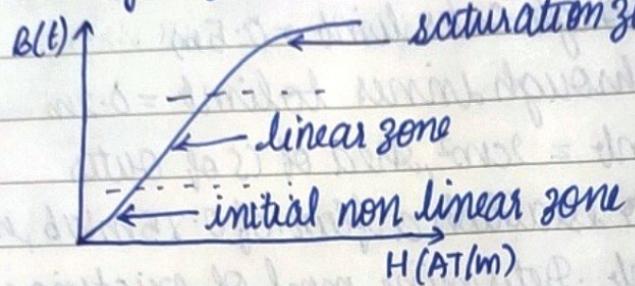

saturation zone μ_r is not constant

$$B = \mu_0 H = M_0 \mu_r H$$

At saturation, $\mu_r = 0$

$$L = \frac{\mu_0 N^2 A}{l} = 0$$

AC Magnetization


$$\phi = \frac{\mu_0 \mu_r A N I}{l g}$$

time varying flux \rightarrow Emf

$$\phi_m \sin(\omega t) = \frac{\mu_0 \mu_r A N I_m \sin(\omega t)}{l g} \quad \text{induced (Lenz's law)}$$

$$E = \frac{d}{dt} (\text{flux linkage}) = \frac{d}{dt} (N \phi) \quad [E=0 \text{ for DC current}]$$
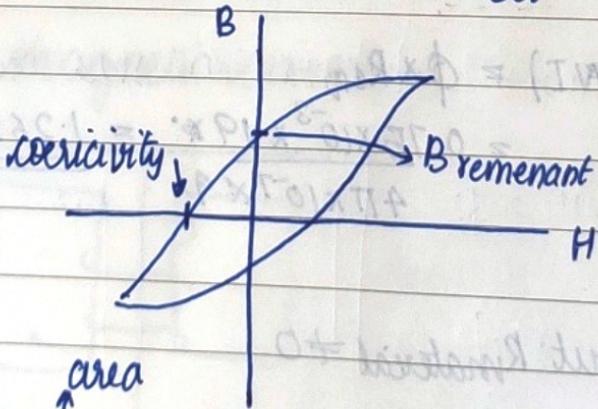
$$E = \frac{d\lambda}{dt} = \frac{d\lambda}{di} \times \frac{di}{dt} = L \frac{di}{dt} \quad \text{as } L = \frac{d\lambda}{di} \quad \text{(flux linkage per unit current)}$$



Area under this hysteresis loop is core loss/hysteresis loss (energy)

$$\text{Power loss} = E \times F \rightarrow \text{frequency}$$

$$P_h = K_h f B_m^n \text{ W/m}^3$$

K_h is a characteristic constant of the core material, B_m is

the maximum flux density and n , called Steinmetz exponent, may vary from 1.5 to 2.5 depending upon material and is often taken as 1.6.

Variation of B-H loop with F : frequency \downarrow area \downarrow , f \uparrow core becomes wide.

Types of B-H loop:

- Narrow for high frequency AC application
- Wide for permanent magnet application

AC core loss :

(i) Eddy current loss \rightarrow due to induced EMF and circulating current. time varying flux \rightarrow induced voltage \rightarrow eddy current \rightarrow loss.

Eddy current loss \rightarrow due to induced EMF and circulating current. Induced EMF proportional to frequency and amplitude of flux. Loss proportional to EMF^2 . Eddy current loss proportional to F^2 .

$$P_e = K_e f^2 B^2 \text{ W/m}^3$$

$$\text{Total core loss} = P_h + P_e = k_1 B^n f + k_2 B^2 f^2$$

- eddy current is low if electrical resistivity of core is high
- core with high resistivity (ferrite), core made with powdered iron. Material divided into thin laminations.

Q: For a material, core loss = 1550W at 50Hz, 3000W at 75Hz
 (keeping Bpeak same). calculate core loss at 100Hz.

$$\text{core loss} = K_1 B^n f + K_2 B^2 f^2$$

$$L = K_1 B^n f + K_2 B^2 f^2$$

$$\frac{L}{f} = K_1 B^n + K_2 B^2 f$$

$$3I = K_1 B^n + K_2 B^2 \times 50$$

$$40 = K_1 B^n + K_2 B^2 \times 75$$

$$3I = A + 50B$$

$$40 = A + 75B$$


$$B = \frac{9}{25}, A = 13$$

$$L = 13 \times 100 + \frac{9}{25} \times 100 \times 100 = 1300 + 3600 = \underline{\underline{4900W}}$$

Application of Magnetic Circuit

- transformer
- electric machines
- Inductors

Magnetic Circuits and Inductance

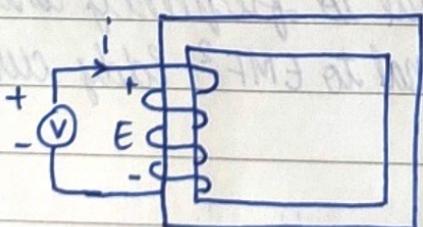

$$V = E = \frac{d\phi}{dt}$$

$$V_m \sin \omega t = N \frac{d\phi}{dt}$$

$$\phi = \frac{\mu_0 M_r N I}{l_g} \rightarrow f(t)$$

$$\phi(t) : E_{mf} = E = N \frac{d\phi}{dt}$$

$$f(t) = \int V dt$$

$$V = L \frac{di}{dt}$$

$$i = \sqrt{\frac{V}{L}} dt$$



$$V = iR + E$$

$$= iR + N \frac{d\phi}{dt}$$

$$\phi = V_m \cos \omega t$$

$$V = 4.44 f m N \Phi$$

rms voltage \downarrow peak flux

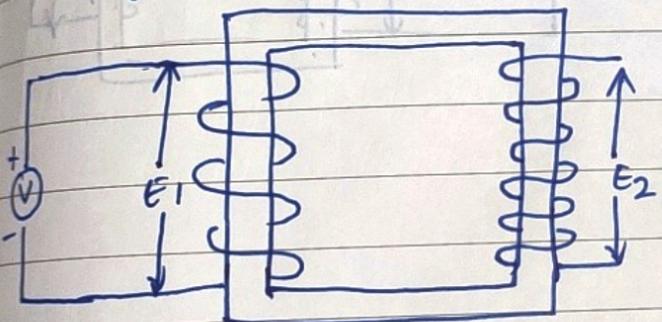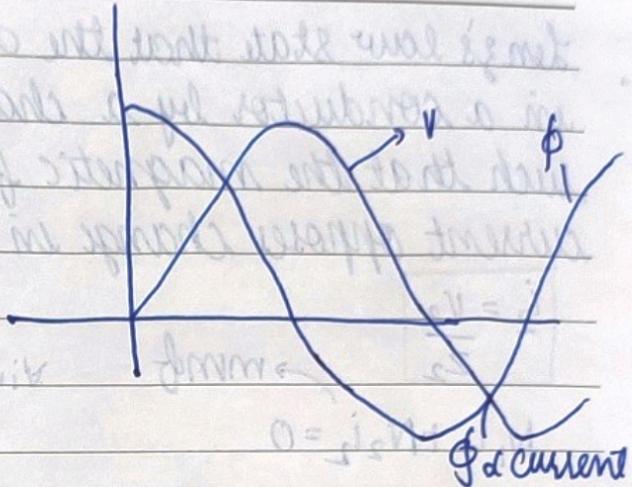

$$E_1 = V = N_1 \frac{d\phi}{dt}$$

$$E_2 = N_2 \frac{d\phi}{dt}$$

$\frac{E_1}{E_2} = \frac{N_1}{N_2}$ (operating principle for a transformer)

$$E_2 = \frac{N_2}{N_1} E_1$$

AC magnetic circuit with two windings

$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$
 only when B is Not saturated

$$\Phi = -\frac{1}{N_1} \int V_1 dt \quad V_2 = -N_2 \frac{d\phi}{dt}$$

$$V_1 = V_m \sin(2\pi f t), \quad V_{1,\text{rms}} = 4.44 f N_1 \Phi_m$$

$$\frac{V_2 \text{ rms}}{V_1 \text{ rms}} = \frac{N_2}{N_1}$$

$$i_1^0 = \frac{V_1 \text{ rms}}{wL}, \quad L = \frac{\mu_0 A \mu_r N_1^2}{l_g}$$

no load current

magnetizing current


Lenz's law states that the direction of the electric current in a conductor by a changing magnetic field is such that the magnetic field created by induced current opposes change in the initial magnetic field.

$$i_2 = \frac{V_2}{Z_2}$$

$$N_1 i_1 + N_2 i_2 = 0$$

$$v_1 = \frac{N_2}{N_1} (-i_2)$$
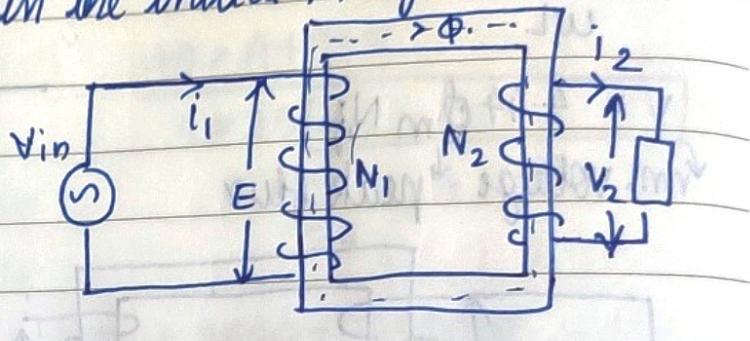
$$\text{But } \phi = -\frac{1}{N_2} \int v_{in} dt$$



Components of primary current

1. Load component $\rightarrow i_1 = N_2 i_2 / N_1$

2. (a) No load magnetizing component (magnetizing current)

(b) no load loss component

$$i_1 = \frac{v_{in}}{w_1} \rightarrow \begin{array}{l} \text{core loss} \\ \downarrow \\ \text{eddy currents} \end{array}$$




\downarrow Depends only on voltage, not on Z_2 or i_2

Reflected impedance:

Impedance connected to secondary, but current drawn on primary.

$$Z'_2 = \frac{V_1}{i'_1} = \frac{V_1}{N_2 / N_1 \times i_2} = \frac{V_1}{N / N_1 \times V_2 / Z_2} = \frac{V_1}{N_2 / N_1 \times N_2 / N (V_1 / Z_2)}$$
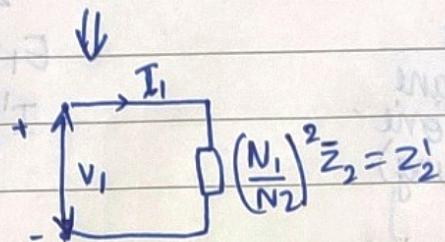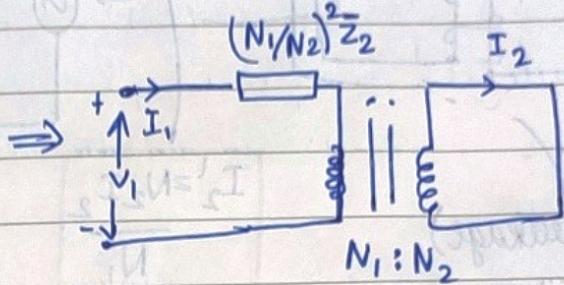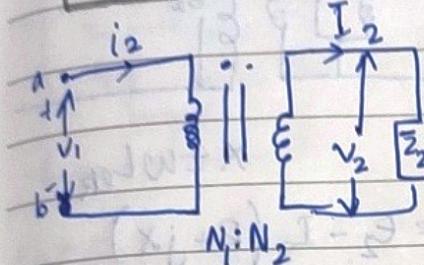
$$\Rightarrow Z'_2 = \frac{N_1^2}{N_2^2} Z_2$$



- Q: For a 150:75 ratio transformer, the primary is connected to 200 V_{rms} source and secondary is connected to a load impedance of $8+6j$. Calculate
 (i) load impedance reflected to primary side
 (ii) secondary and primary current
 (iii) Primary and secondary side real and reactive power


ans: (i) $Z'_2 = \left(\frac{N_1}{N_2}\right)^2 Z_2 = \left(\frac{150}{75}\right)^2 (8+6j) = \underline{\underline{32+24j}}$

(ii) $V_1 = 200V, V_2 = (N_2/N_1)V_1 = (75/150) \times 200 = 100V$


$$i_2 = V_2/Z_2 = 100/(32+24j) = (2-3/2j)A$$

$$i_1 = -(N_2/N_1) \times i_2 = (2-3/2j/2) = (1-3/4j) A$$

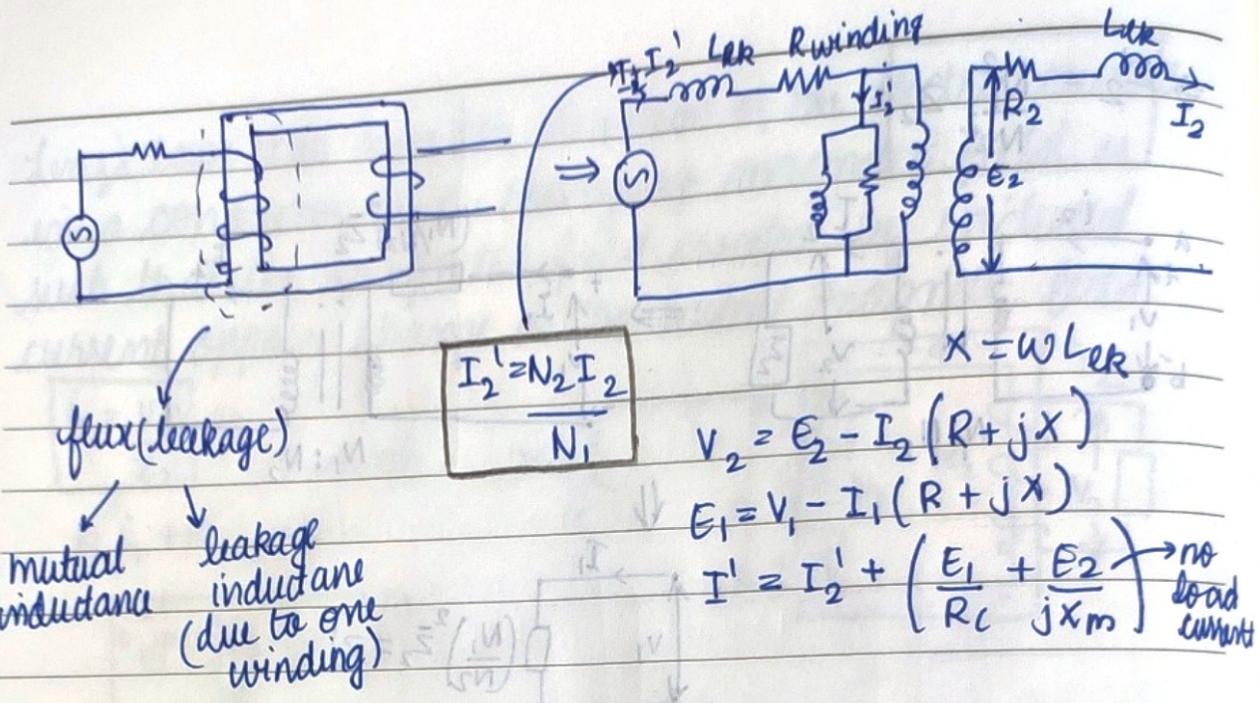(iii) $P_2(\text{real}) = i_2^2 \text{Real}(Z_2) \Rightarrow P_2(\text{real}) = i_2^2 \text{Real}(Z'_2)$ both are equal.
 reactive power $50W$ \downarrow modulus value \downarrow (rms value in formula) \downarrow reactive $= i_{\text{rms}}^2 \times$ \rightarrow imaginary part of impedance
 $Q_1 = 37.5W$ $Q_2 = 37.5W$



Components of equivalent circuit

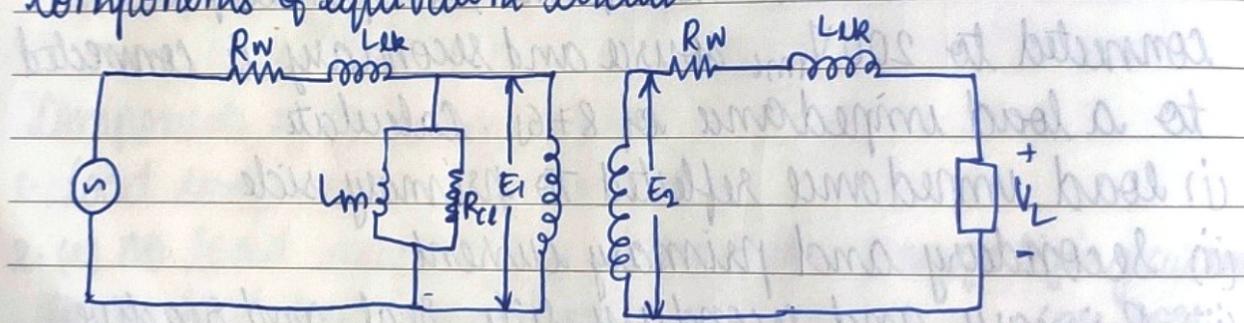

$R_W \rightarrow$ Winding resistances

$L_{RK} \rightarrow$ leakage inductances

$L_m \rightarrow$ Magnetizing inductances

$R_{CL} \rightarrow$ Core loss resistance

Adeal transformer:

$$i_o = 0$$


$$R = 0$$

$$L_{RK} = 0$$

$$L_m = \infty$$

$$R_{CL} = 0$$

Shunt Branch (No load current)

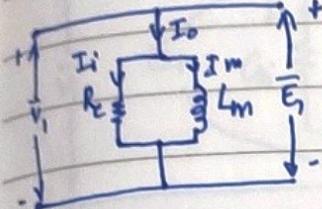

- No load current only depends on applied voltage and frequency.

$$I_o = I_m + I_i$$

$$I_o = \frac{E_1}{j\omega L_m} + \frac{E_1}{R_c} \approx \frac{V_1}{j\omega L_m} + \frac{V_1}{R_c}$$

$$L_m = \frac{\mu_0 M_{max} N_1^2 \lg}{A}$$


$$R_c = \frac{V_1^2}{P_{ironloss}}$$

- R is a function of applied voltage and frequency due to dependence of hysteresis and eddy current loss on B and F .
- Shunt branch also represented as shunt admittance, $G + jB$

$$G - jB = \frac{1}{R} + \frac{1}{j\omega L_m}$$

$$\vec{I}_o = \vec{I}_i + \vec{I}_m$$

$$|I_o| = \sqrt{I_i^2 + I_m^2}$$

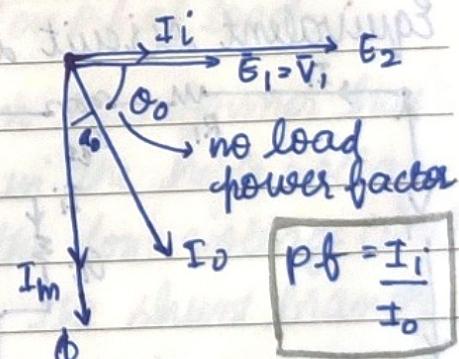

- for ideal transformer: $I_o = 0$ as $R_c, L_m \rightarrow \infty$

Q: A transformer on no load has a core loss of 50W, draws a current of 2A (rms) and has an induced emf of 230V (rms), 50Hz. Determine the core-loss current, magnetizing current and no load power factor. calculate the no load circuit parameters of the transformer (R_c and L_m) (Neglect winding resistance and leakage flux).

$$P_f = \frac{50}{2 \times 230} = 0.108 \quad I_i = I_o \times P_f = 0.217 A$$

$$I_m = I_o \sin \theta = 2 \times \sin(\cos^{-1}(P_f)) = 1.988 A$$

No. load power factor: $P_f = 0.108$


$$R_C = \frac{V_1^2}{\text{Power loss}} = \frac{230 \times 230}{50} = 1.058 k\Omega$$

$$B_m = \frac{I_m}{V_1} = \frac{1.988}{230} = 8.64 \times 10^{-3} V$$

$$B_m = \frac{1}{\omega L_m} \Rightarrow L_m = \frac{1}{\omega B_m} = \frac{1 \times 230}{100\pi \times 1.988} = 0.368 H$$

$$R_C = 1.058 k\Omega, B_m = 0.368 H$$

Equivalent circuit of transformer

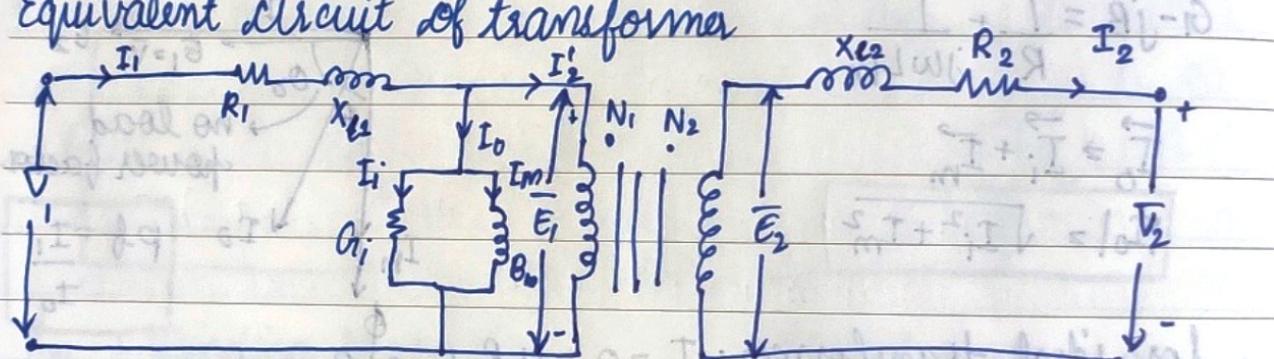


$$\bar{V}_1 = \bar{E}_1 + \bar{I}_1 R_1 + j \bar{I}_1 X_1 \rightarrow \text{leakage resistance}$$

$$\bar{V}_2 = \bar{E}_2 - \bar{I}_1 R_2 - j \bar{I}_2 X_2 \quad E_2 = \frac{N_2}{N_1} E_1$$

$$R'_2 + j X'_2 = \left(\frac{N_1}{N_2} \right)^2 (R_2 + j X_2) \quad I'_2 = \frac{N_1}{N_2} I_1, \quad I_1 = I'_2 + I_0 - \text{no load current}$$

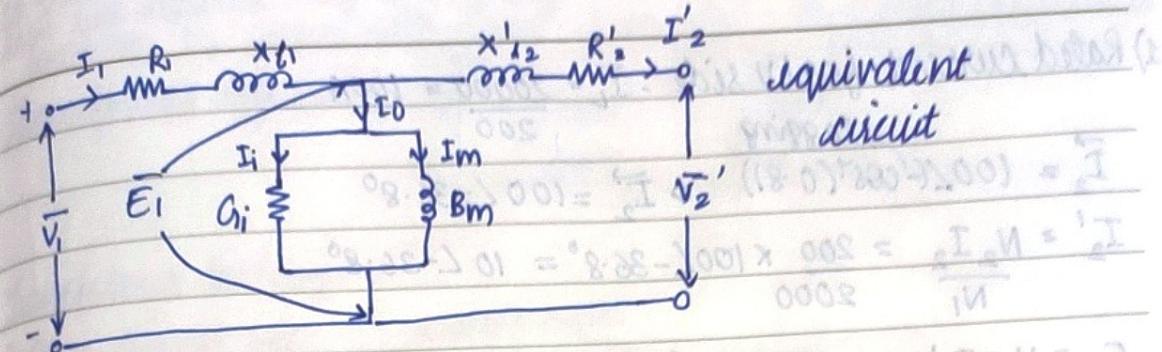Dashed quantities are referred quantities.



Transformer ratings: for continuous operation

• voltage rating (depends on core)

• voltage ratio $= 2000/200 = 10$ primary/secondary


• frequency rating

• current rating

• VA rating depends on conductor power but written VA as it doesn't depend on P.F. of load

Q: A 20kVA, 50Hz, 2000/200V distribution transformer has a leakage impedance of $0.42 + j0.52$ in the high voltage (HV) winding and $0.004 + j0.05$ in the low voltage (LV) winding. When seen from HV side, the shunt branch admittance Y_0 is $(0.002 - j0.015)$. If the sending-end voltage applied to the transformer is 2kV, the load is drawing rated transformer current at 0.8 pf lagging.

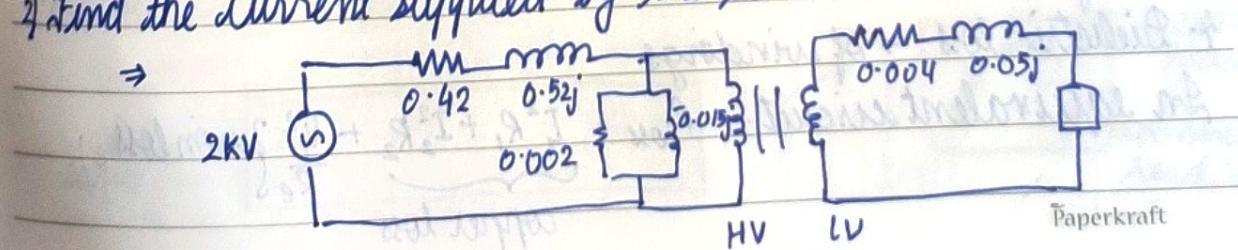1) Find the voltage at the load-end of the transformer
2) Find the current supplied by the source



1) Rated current for LV side : $I_L = \frac{20000}{200} = 100A$

$$\vec{I}_2 = 100 \angle -36.8^\circ \text{ lagging} \Rightarrow \vec{I}_2 = 100 \angle -36.8^\circ$$

$$I_2' = \frac{N_2}{N_1} I_2 = \frac{200}{2000} \times 100 \angle -36.8^\circ = 10 \angle -36.8^\circ$$

$$E_1 = V_1 - I_2' Z = 2000 - (0.42 + 0.52j) \times 10 \angle -36.8^\circ$$

$$= 1993.5 \angle 0.471^\circ$$

$$E_2 = \frac{N_2}{N_1} E_1 = 199.35 \angle 0.471^\circ$$

$$V_2 = E_2 - I_2 Z_2 = 199.35 \angle 0.471^\circ - (100 \angle -36.8^\circ \times (0.004 + 0.05j))$$

$$= 196.07 \angle -1.47^\circ$$

2) $I_o = E_1 \times Y_o = 1993.5 \angle 0.471^\circ (0.0002 - 0.0015j)$
 $= 0.423 - 2.987j$

$$I_s = I_o + I_2' = 0.423 - 2.987j + 8.007 - 5.99j$$

$$= 8.43 - 8.98j = 12.315 \angle -46.8^\circ$$

Transformer losses (decreases efficiency and increases temperature)

1. Core loss (Hysteresis & eddy current) → depends on induced voltage
2. Copper loss → 0 for no load (depends on current)
3. Stray loss → due to mutual
4. Dielectric loss → of windings

In equivalent circuit:


$$P_{loss} = \underbrace{I_1^2 R_1 + I_2^2 R_2}_{\text{copper loss}} + \frac{V_1^2}{R_{eq}} \text{ iron loss}$$

* $P_{\text{load}} = V_2 I_2 \cos(\phi_2) = S \cos(\phi_2)$, V_2 varies slightly with loading, so variation of V_2 with load can be neglected for efficiency calculation. Iron loss depends only on voltage, so it remains constant with loading. I_2 varies with load linearly. $\phi_2 \rightarrow$ load parameter.

Transformer efficiency: $\eta = \frac{P_{\text{output}}}{P_{\text{input}}} = \frac{P_{\text{load}}}{P_{\text{load}} + \text{losses}}$

Transformer testing:

(i) Open circuit test

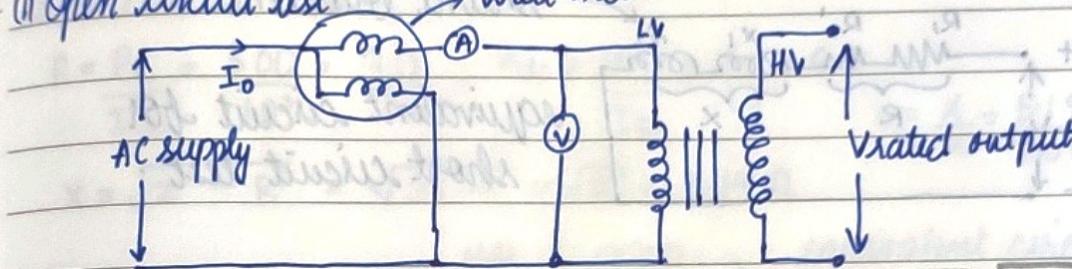


Ammeter reading: no load current : $I_m = \sqrt{I_o^2 - I_i^2}$, $I_i = V_1 / R_c$


Watt meter reading: iron loss (core loss)

$$R_c = \frac{V_1^2}{P_0}$$

$$I_m = \frac{V_1}{wL_m}$$

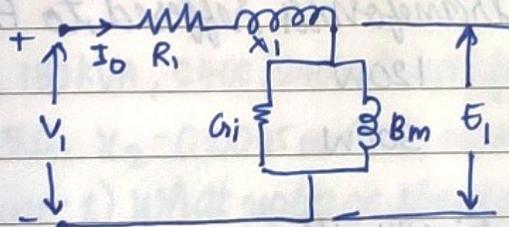


Current only flows through shunt part

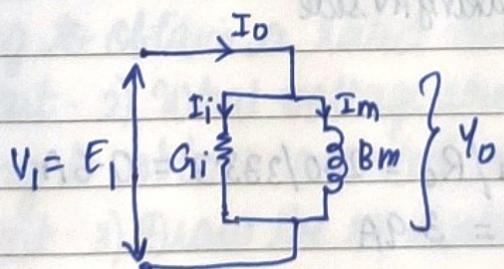

Equivalent circuit for open circuit test

(ii) Short circuit test

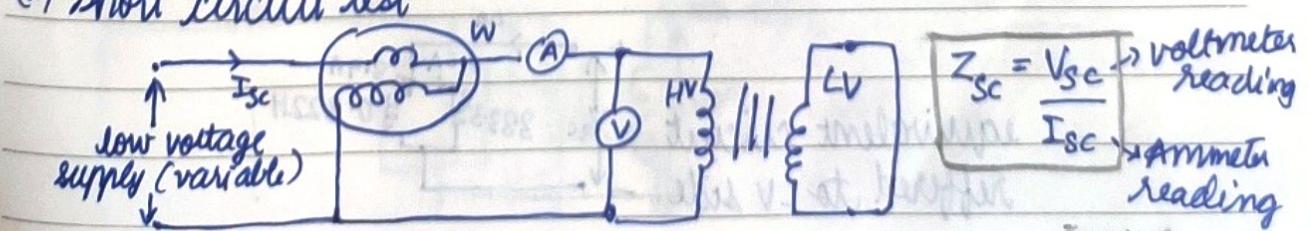


$$Z_{sc} = \frac{V_{sc}}{I_{sc}}$$

voltmeter reading
ammeter reading

Paperkraft

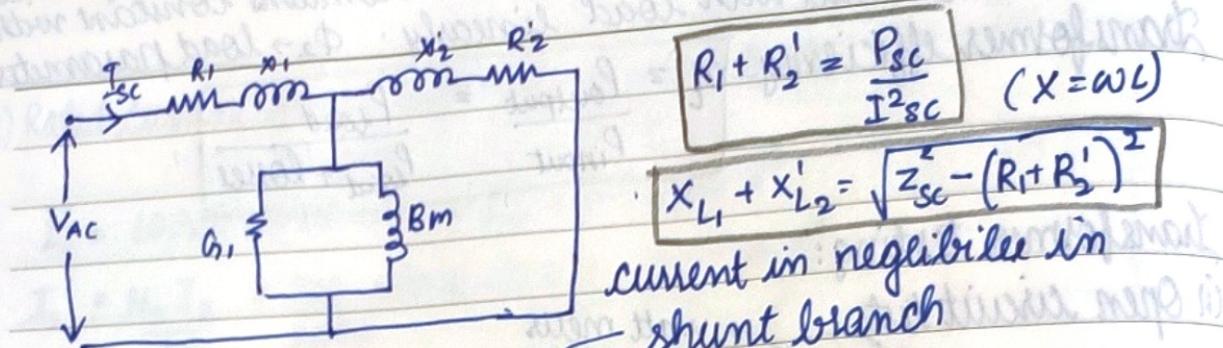
gratitud. Ahora juntamos el circuito. $(\phi)_{SC} = (\phi)_{OC} \cdot 2 = (\phi)_{OC} I_{SC} V = 100 \cdot 9 \cdot 2$



$$R_1 + R_2' = \frac{P_{SC}}{I_{SC}^2} \quad (X = \omega L)$$

$$X_{L1} + X_{L2}' = \sqrt{Z_{SC}^2 - (R_1 + R_2')^2}$$

current in negligible in
shunt branch

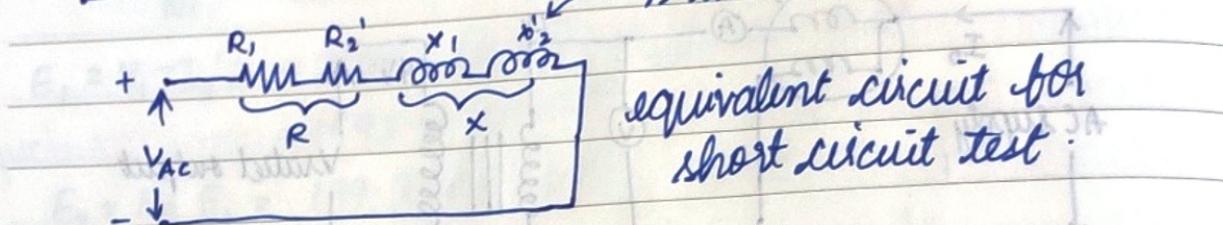

equivalent circuit for
short circuit test

Q: The following data were obtained on a 20kVA, 50Hz, 2000/200V distribution transformer. Draw the approximate equivalent circuit of the transformer referred to HV side.

OC test 200V 4A 120W

SC test 60V 10A 300W


Open circuit test:

$$R_C = \frac{V_1^2}{P_0} = \frac{200 \times 200}{120} \rightarrow \text{taking HV side}$$

$$R_C = 333.3 \Omega, I_i = V_1 / R_C = 200 / 333.3 = 0.6 A$$

$$I_m = \sqrt{I_o^2 - I_i^2} = \sqrt{4^2 - 0.6^2} = 3.9 A$$
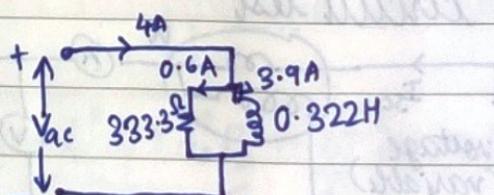
$$L_m = \frac{V_1}{W I_m} = \frac{200}{100 \pi \times 3.9} = 0.322 H$$




equivalent circuit
referred to LV side

$$R_{HV} = \left(\frac{N_1}{N_2}\right)^2 \times 333.3 = \cancel{83.3k\Omega} \quad 0.3\Omega$$

~~0.322 mH~~
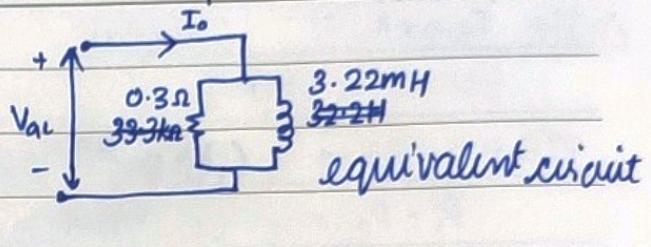
$$L_{HV} = \left(\frac{N_1}{N_2}\right)^2 \times 0.322 H = \cancel{32.2H}$$




short circuit test

$$R = P_{SC} = \frac{300}{10^2} = \underline{\underline{3\Omega}}, \quad Z_{SC} = \frac{V_{SC}}{I_{SC}} = \frac{60}{10} = 6\Omega$$

$$L_m = \frac{X}{\omega} = \frac{5.19}{100\pi} = \underline{\underline{16.5mH}}$$
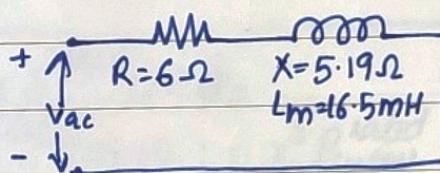
$$X = \sqrt{Z^2 - R^2} = \sqrt{36 - 9} = \sqrt{27} = 5.19\Omega$$




equivalent circuit
for short circuit
test.

Q: For a 150 kVA, 2400/240V transformer, $R_1 = 0.2\Omega$, $R_2 = 0.002\Omega$, $X_1 = 0.45\Omega$, $X_2 = 0.0045m\Omega$, $R_i = 10k\Omega$, $X_m = 1600\Omega$.

Determine: 1) what voltage should be applied at the LV winding to obtain a rated voltage at the HV terminals in OC test. 2) What voltage should be applied at the HV winding to obtain a rated current at the LV terminal in SC test. 3) Draw the equivalent circuit indicating values in PU.

Open circuit:

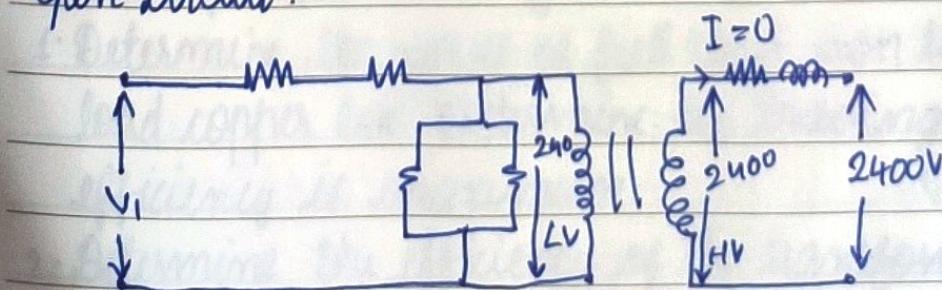

Transformer efficiency:

at x times rated load:

$$\text{load at } (x \text{ times rated load}) = x S^{\text{rated}} \cos(\phi_2)$$

$$I_2 \text{ at } (x \text{ times rated load}) = x I_2^{\text{rated}}$$


$$\text{P}_{\text{cu loss}} \text{ at } (x \text{ times rated load}) = x^2 P_{\text{cu loss}}^{\text{rated}}$$

$$\eta(x) = \frac{P_{\text{load}}(x)}{P_{\text{load}}(x) + P_{\text{cu loss}}(x) + P_{\text{iron loss}}(x)}$$

$$\boxed{\eta(x) = \frac{x S^{\text{rated}} \cos(\phi_2)}{x S^{\text{rated}} \cos(\phi_2) + x^2 P_{\text{cu loss}}^{\text{rated}} + P_{\text{iron loss}}^{\text{rated}}}}$$

for maximum efficiency, $\frac{d(\eta(x))}{dx} = 0$
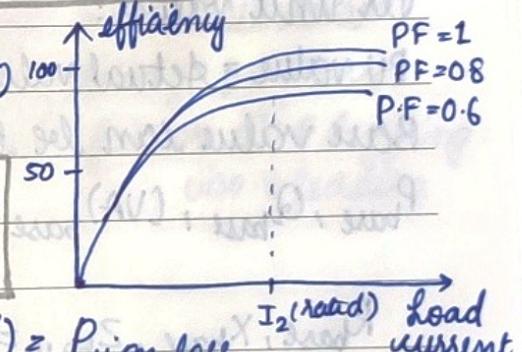
$$x = \sqrt{\frac{P_{\text{iron loss}}^{\text{rated}}}{P_{\text{cu loss}}^{\text{rated}}}} = x_{\text{max-efficiency}}$$



$$\text{P}_{\text{cu loss}} \text{ at } (x_{\text{max-efficiency}} \text{ times rated load}) = P_{\text{iron loss}}$$

Q: A 500kVA transformer has an efficiency of 95% at full load and also at 60% full load; both at upf

1. Determine the values of full load iron loss and full load copper loss. Determine the loading at which efficiency is maximum.

2. Determine the efficiency of the transformer at $\frac{3}{4}$ th full load.

$$1) \eta = \frac{500 \times 1}{500 \times 1 + P_i + 0.36 P_c} = 0.95$$

$$0.95 = \frac{500 \times 0.6}{500 \times 0.6 + P_i + 0.36 P_c}$$

$$475 + 0.95 P_i + 0.95 P_c = 500 \quad 285 + 0.95 P_i + 0.342 P_c = 300$$

$$P_i + P_c = 25 / 0.95$$

$$\Rightarrow 0.608 P_c = 10 \quad P_c = 10 / 0.608 = \underline{\underline{16.45 \text{ kW}}}$$

$$\Rightarrow P_i = 25 / 0.95 - 10 / 0.608 = \underline{\underline{9.87 \text{ kW}}}$$

$$2) \eta = \frac{500 \times 0.75}{500 \times 0.75 + 9.87 + 16.45 \times (0.75)^2}$$

$$= \frac{375}{375 + 9.87 + 9.253125} = 0.9515 = \underline{\underline{95.15\%}}$$

Per unit values:

PU value = Actual value / Base value

Base value can be taken as rated value.


$$P_{\text{base}}, Q_{\text{base}}, (VA)_{\text{base}} = V_{\text{base}} I_{\text{base}}$$

$$R_{\text{base}}, X_{\text{base}}, Z_{\text{base}} = \frac{V_{\text{base}}}{I_{\text{base}}}, \frac{V_{\text{base}}^2}{(VA)_{\text{base}}}$$

Voltage regulation

$$\% \text{ voltage regulation} = \frac{|V_2(\text{no load}) - V_2(\text{full load})| \times 100}{|V_2(\text{no load})|}$$
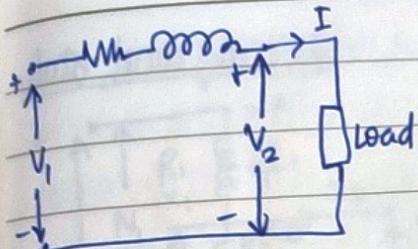
$$\% \text{ voltage regulation} = \frac{V_2(\text{no load}) - V_2(\text{full load}) \times 100}{V_2(\text{full load})}$$



$$V_{20} = V_1$$


$$V_{20} - V_2 = I(R \cos \phi \pm X \sin \phi)$$

$(V_{20} \rightarrow V_2 \text{ when } I \text{ is } 0)$


$$\% \text{ Voltage regulation, Reg} = \frac{V_{20} - V_2}{V_2} \times 100$$

$$\Rightarrow \text{Reg} = \frac{V_{20} - V_2}{V_2} \times 100$$

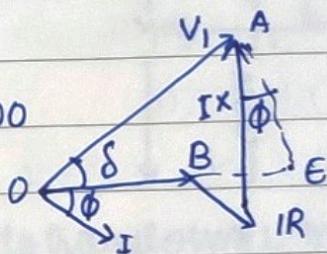
$$= \frac{I(R \cos \phi \pm X \sin \phi)}{V_2} \times 100$$



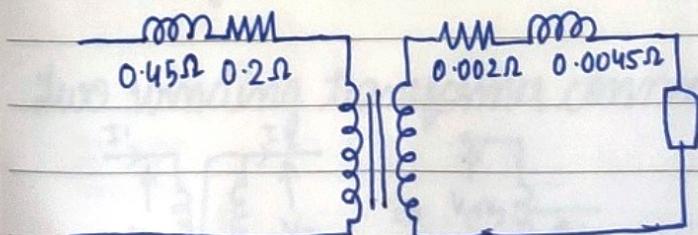
Q: For a 150 kVA, 2400/240V transformer, $R_1 = 0.2 \Omega$, $R_2 = 0.002 \Omega$, $X_1 = 0.45 \Omega$, $X_2 = 0.0045 \Omega$ with full-load on the LV side at rated voltage, calculate the excitation voltage on HV side and voltage regulation. The load power factor is (i) 0.8 lagging. (ii) 0.8 leading.



auto transformer

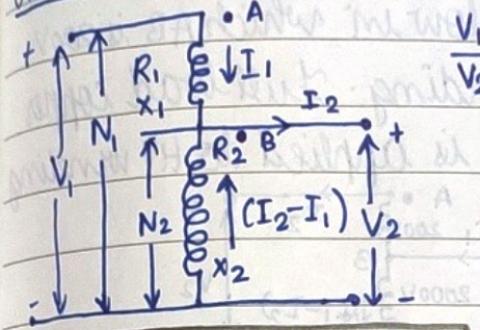

$$\frac{V_1}{V_2} = \frac{N_1}{N_2}$$

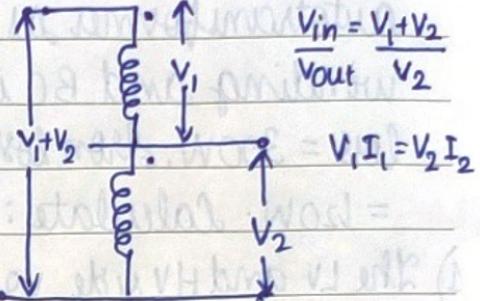

$$\frac{V_{in}}{V_{out}} = \frac{V_1 + V_2}{V_2}$$

$$V_1 I_1 = V_2 I_2$$

$$(VA)_{upper} = (V_1 - V_2) I_1$$

$$(VA)_{lower} = V_2 (I_2 - I_1)$$

for auto transformer VA rating is reduced


$$\text{load(VA)} \leq \text{transformer(VA)}$$

Required ratings are reduced, so a given 2 winding transformer rated for S can be operated to load higher than S if connected as an auto transformer.

Disadvantage : No isolation between input and output

Advantages : can connect a higher load, saves copper

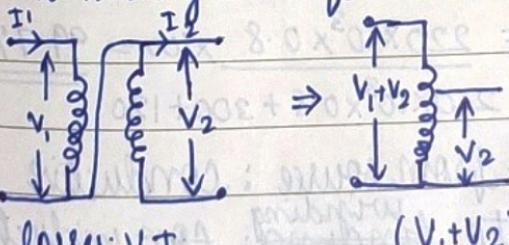Two winding transformer connected as auto transformer



$$(V_1 + V_2) I_1 = V_2 I_2$$

losses: $V_1 I_1$

Q: A 2000/200-V, 20-kVA autotransformer is connected as a step-up autotransformer as in figure below in which AB is 200V winding and BC is 2000-V winding. Full load copper loss = 300W. Iron loss when 2000V is applied to HV winding = 120W. Calculate:

1) The LV and HV side voltage ratings of the autotransformer.

2) KVA rating of autotransformer.

3) efficiency at full load 0.8 pf

4) KVA transferred inductively and conductively

$$\text{ans: 1) LV voltage} = \underline{\underline{2000\text{V}}}$$

$$\text{HV voltage} = \underline{\underline{2200\text{V}}}$$

$$2) \text{KVA} = V_2 I_2 = 2200 \times I_2$$

$$I_2 = \frac{20000}{200} \rightarrow 100 \text{ A (step up rated voltage)}$$


$$\Rightarrow \text{KVA} = 2200 \times 100 = \underline{\underline{220 \text{ kVA}}}$$

$$3) \eta = \frac{P_{\text{load}}}{P_{\text{load}} + P_{\text{copper}} + P_{\text{iron}}} = \frac{220 \times 10^3 \times 0.8}{220 \times 10^3 \times 0.8 + 300 + 120} \times 100 = \underline{\underline{99.7\%}}$$

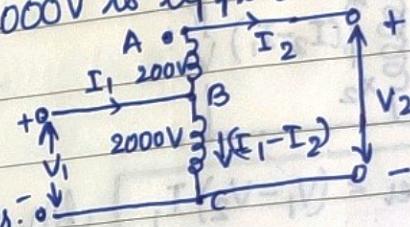4) The power transferred directly from source : conductive power transferred directly to ~~winding~~: core inductive



$$P_{\text{KVA conduct}} = 2000 \times I_1 = 2000 \times 10 = 20 \text{ kVA (common)}$$

$$P_{\text{KVA induc}} = 200 \times I_2 = 200 \times 100 = 20 \text{ kVA (not common)}$$





Three phase transformer

Y-Y (Star - Star)

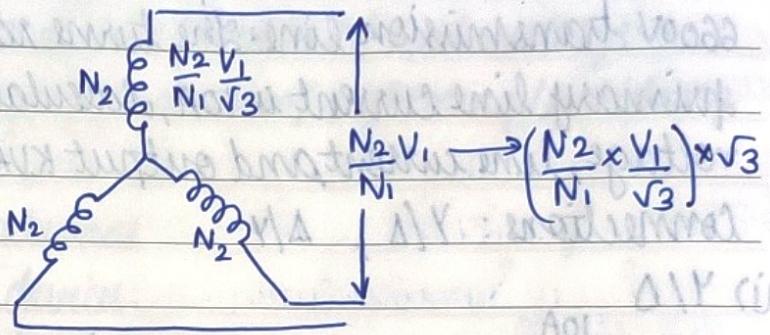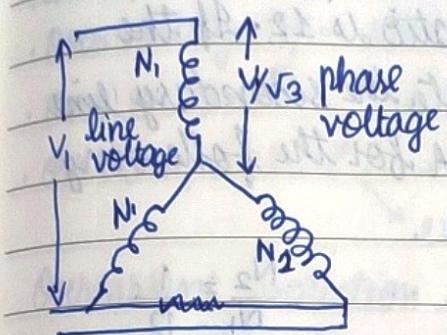


Δ-Δ (Delta - Delta)

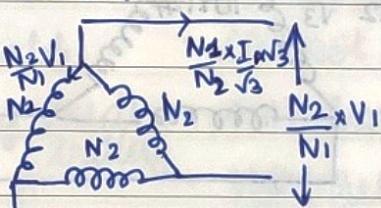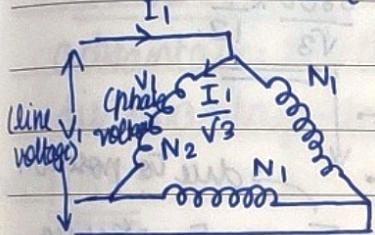

* Star connection - voltage rating is reduced


* Delta connection - current rating is reduced.

Star-Delta (Y-Δ)

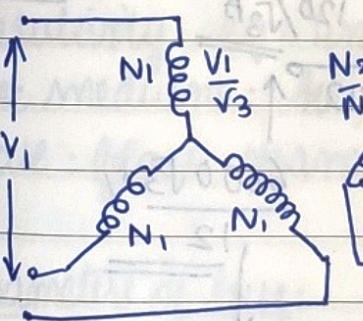

secondary side line voltage lags primary side line voltage by 30°

Delta-Star (Δ-Y)


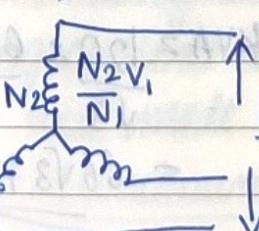


secondary side line voltage leads primary side line voltage by 30°

Paperkraft



Q: A 3-phase transformer bank consisting of three 1-phase transformers is used to stepdown the voltage of a 3-phase 6600V transmission line. The turns ratio is 12. If the primary line current is 10A, calculate the secondary line voltage, line current and output KVA for the following connections: Y/Δ, Δ/Y

(i) Y/Δ

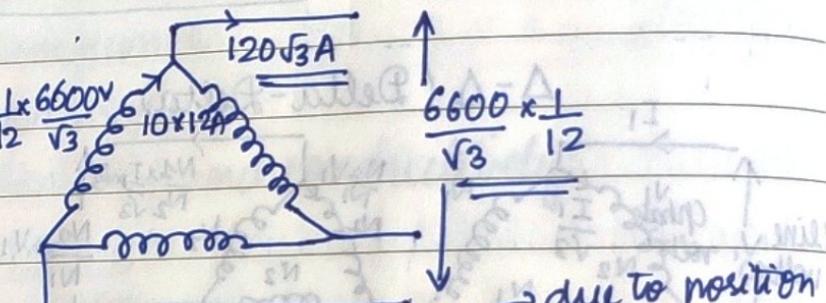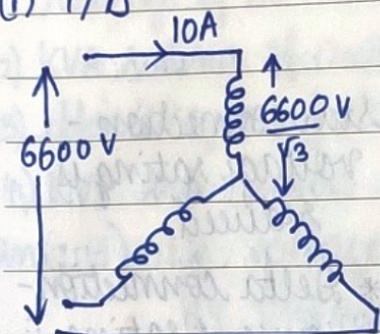

$$\text{Output KVA} = \frac{6600}{\sqrt{3}} \times \frac{1}{12} \times 120\sqrt{3} = \underline{\underline{66\sqrt{3} \text{ KVA}}}$$

(ii) Δ/Y

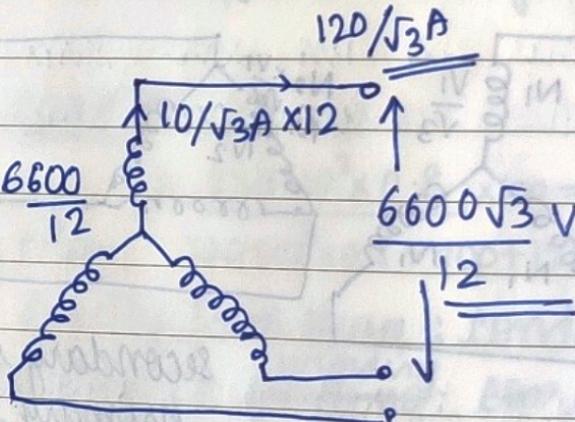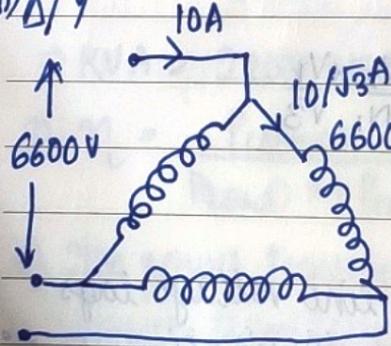

$$\begin{aligned}\text{Output KVA} &= \frac{120}{\sqrt{3}} \times \frac{6600}{\sqrt{3}} \times \frac{1}{12} \times \sqrt{3} \\ &= \underline{\underline{66\sqrt{3} \text{ KVA}}}\end{aligned}$$

Circuit protection devices

circuit Abnormal conditions:

- over voltage → short circuit / overload / undervoltage
- over current → supply fluctuation / lightning / switching
- over temperature → internal
 external

Overcurrent protection devices:

- fuse: advantage - cheap, automatic, fast, disadvantage: threshold current is not precise
- circuit breaker:
 - advantage: resettable
 - disadvantage: lag, needs battery
 - cannot be synchronized (non-controllable)
 - not smart (no indication)
 - non resettable


FUSE:

Components of fuse:

- fuse wire: material with low melting point & high resistivity eg: Tin, lead, zinc
- Arc medium: air, vacuum, Quartz powder
- case: glass, ceramic

Parameters of fuse:

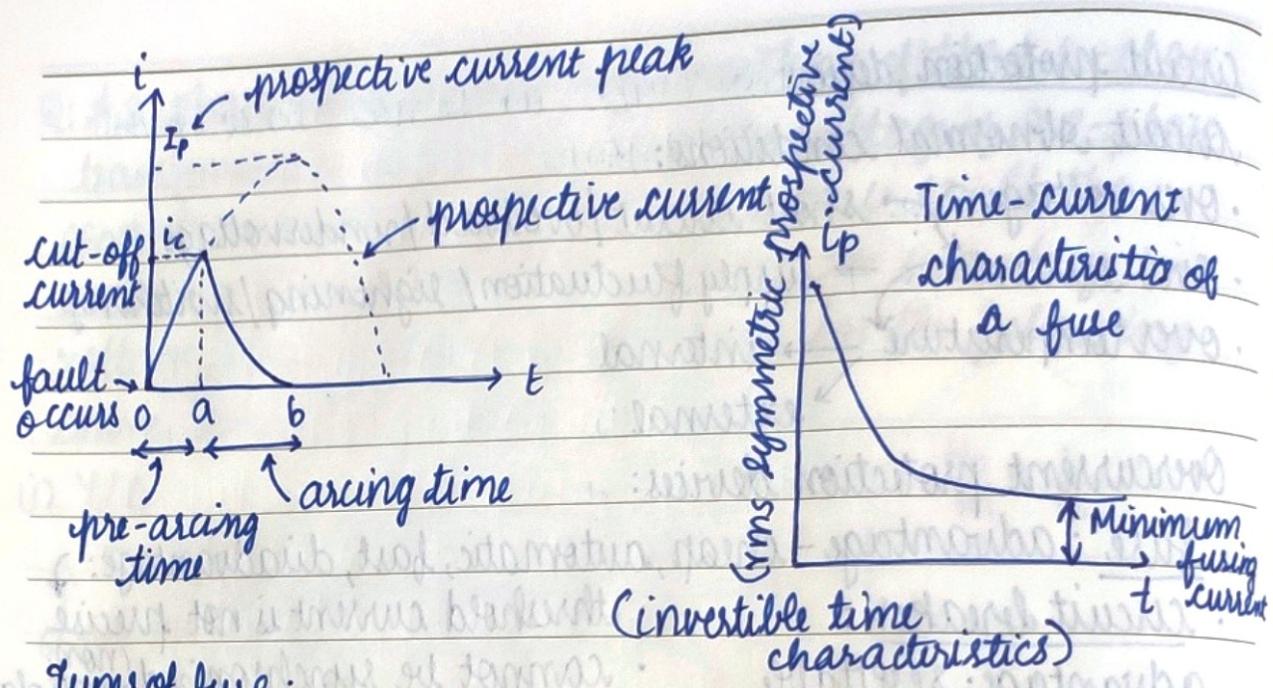- Rated current - current it can carry (maximum) continuously for a long time.
- Minimum fusing current: Minimum rms value current at which fuse will melt. $I = Kd^{1.5}$
- Fusing factor = $\frac{\text{Minimum fusing current}}{\text{rated current}}$




Types of fuse :

- Rewirable (open or semi enclosed)
- Enclosed or cartridge fuse - possible to explode at high current
- high rupturing capacity fuse - industrial application or distribution network for high current
- Expulsion type high voltage fuse - poles for distribution network.

Fuse rating

- current rating - before fuse melts
- I^2t rating
- voltage rating - after fuse melts, depends on arc medium & case
- temperature
- voltage drop

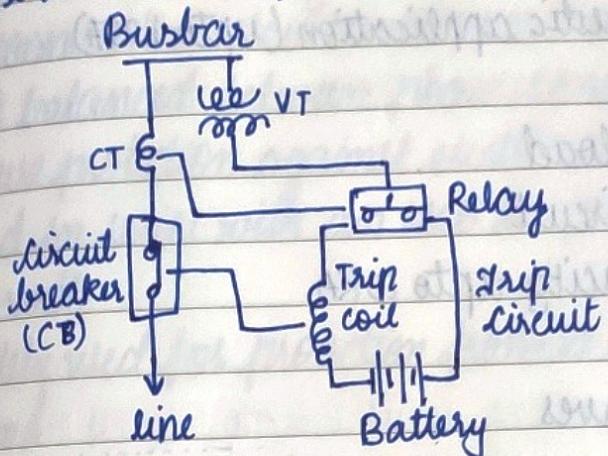Circuit Breaker: Switch which can be used to open or close circuit in power network.



Events during fault clearing

- 1) fault initiation
 - 2) Trip coil energization
 - 3) Opening of contacts
 - 4) Arc extinction
- circuit breaker is slower than fuse

Parameters of circuit breaker:

- Rated voltage (V_n)
- Rated current (I_n)
- Short circuit trip current setting (I_m)
 - ↑ threshold
 - ↓ over load
- short circuit breaking current capacity (I_{cu}/I_{cn})

Types of Circuit Breaker in low voltage network:

• Miniature circuit breaker (MCB)

* for lower current / domestic application (upto 125A)

* Reset very fast

* Bimetallic strip - over load

* Magnetic coil - short circuit

* Interrupt current capacity upto 10KA

* Non adjustable

* Characterized by i-t curves

* MCB trip curves:

→ Z: Trips at 2 to 3 times rated current suitable for highly sensitive applications eg: semiconductor devices

→ B: Trips 3 to 5 times rated current

→ C: Trips at 5 to 10 times rated current suitable for medium inrush current eg: motors, transformers

→ K: Trips at 10 to 14 times rated current suitable for loads with high inrush current

→ D: Trips at 10 to 20 times rated current - suitable for high starting currents.

• Molded case circuit breaker (MCCB)

* for current higher than MCB (upto 1600A)

* Adjustable over load setting

* Interrupt capacity upto 85KA

* Industrial application

- Residual Current Circuit Breaker (RCCB)
 - * Detects and trips against electrical leakage currents
 - * Disconnects the circuit whenever there is a current which is not balanced between phase conductor & neutral.
 - * Ensure protection against electric shock caused by direct contact
 - * Used in series with an MCB to provide overcurrent protection as well.
 - * Widely used for protection from a leakage current of 30, 100 & 300mA.
- Earth Leakage Circuit Breaker (ELCB) → replaced by RCCB&SFU
 - * Voltage operated earth leakage device
 - * Measure the voltage on the earth conductor; if this voltage is not zero this indicates a current leakage to earth.


switch fuse unit:

- Switch plus fuse enclosed in a metal unit
- Can manage only one load at a time
- has ON/OFF option
- overload protection
- available as 2 pole, 3 pole, 4 pole

Wire & cables :

- wire is one electrical conductor while cable is multiple conductors or a group of wires enclosed in sheathing.
- current rating → thickness, insulation, temperature, environment
- voltage rating
- temperature rating
- resistance per unit length
- inductance & capacitance per unit length (at HF)
- Wires → single strand, multi strand, enamel wire

Electrical Machines

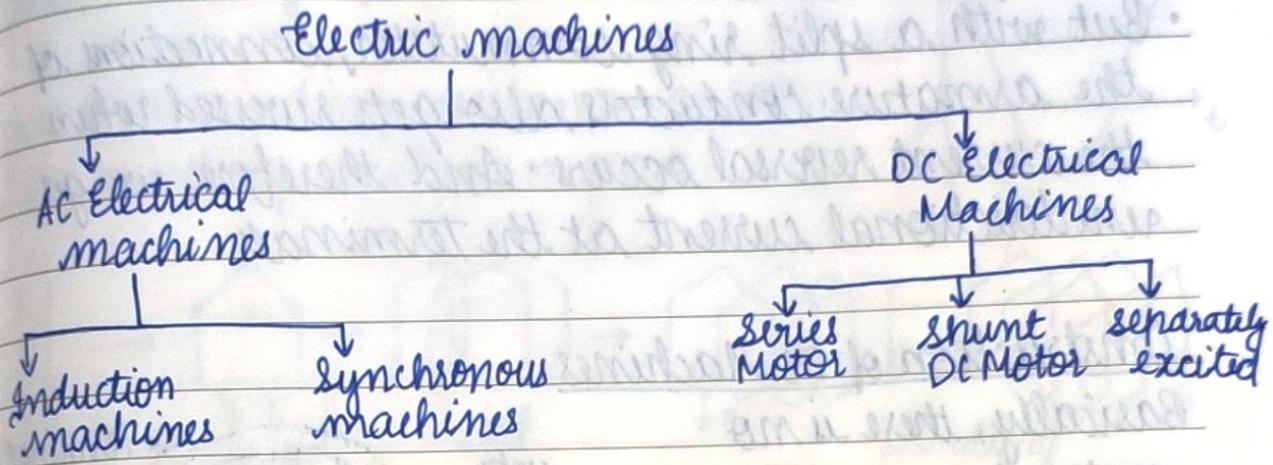

- DC Machines works on Faraday's law of electromagnetic induction principle, which states that a conductor cut the magnetic lines of forces then an electromagnetic force will be induced within the conductors.
- According to Flemings rule, the direction of induced current changes whenever the direction of motion of the conductor changes. Let's consider an armature rotating clockwise and a conductor at the left is moving upward. When the armature rotates completes a half rotation, the direction of motion of that particular conductor will be reversed to downward. Hence, the direction of motion of that current in every armature conductor will be alternating. If you look, you will know how


the direction of the induced current is alternating in an armature conductor.

- But with a split ring commutator, connections of the armature conductors also gets reversed when the current reversal occurs. And therefore, we get unidirectional current at the terminals.

Construction of DC Machines

Basically, there is no constructional difference between a DC motor and

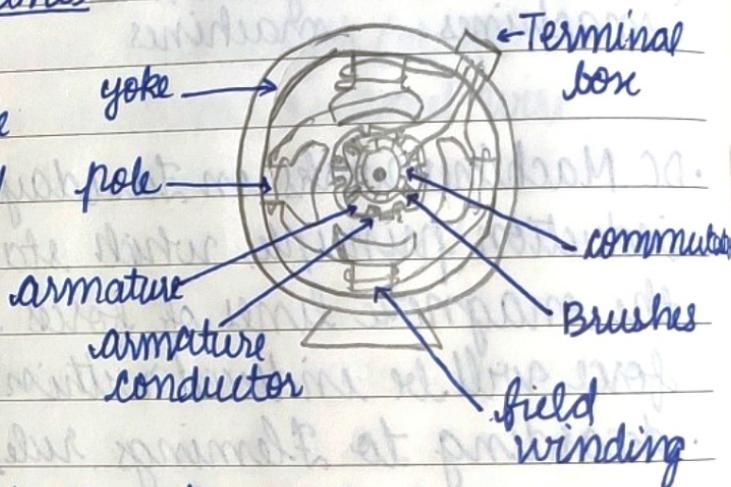a DC generator. The same DC machine can be run as a generator or motor.



DC machines: field winding & armature winding



The rotor has been classified into two parts: lap winding
armature winding & wave winding

- Current rating of the machine depends on the number of parallel paths

Armature can be connected as wave winding, in this case.


armature winding - torque
field winding - flux

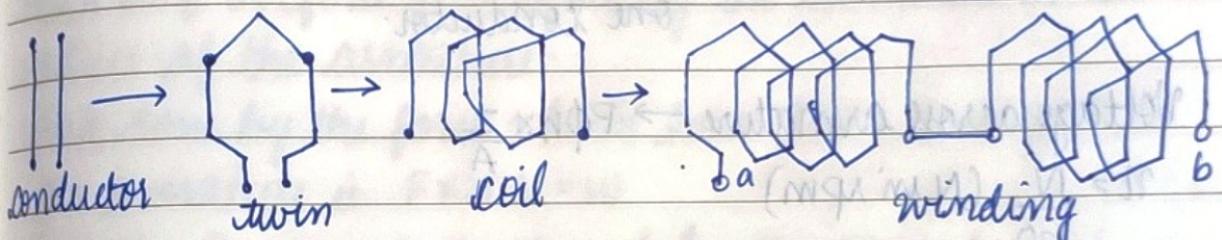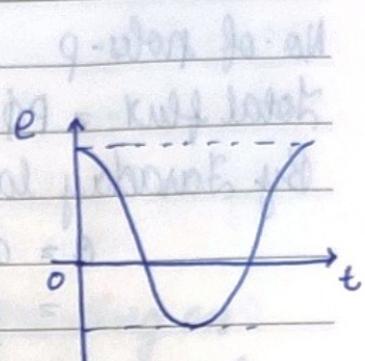armature winding resistance $\rightarrow 0-30\Omega$
field winding resistance $\approx 500\Omega$



lap connection - winding which folds back
the value of parallel path (a) = No. of poles

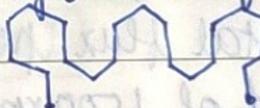Wave connection - winding doesn't fold back, it goes on continuously



No. of parallel paths in case of wave connection (a) = 2

EMF equation of DC Machine

Flux (Φ) (flux per pole)

No. of conductors (z) (No. of conductors in the machine)

A - no. of parallel paths

Speed of armature (n in rps)

No. of conductors in each parallel path = z/A

No. of poles - P

Total flux = $P\phi$

By Faraday law of EMF

$$e = \frac{d\phi}{dt}$$

$$= \frac{P\phi}{\frac{1}{n}} = P\phi n$$

↑ voltage induced in
one conductor.

n revolution in 1 sec

1 revolution $\frac{1}{n}$ sec

Voltage across armature $\rightarrow P\phi n \times \frac{Z}{A}$

$$n = \frac{N}{60} \text{ (N in rpm)}$$

$$\boxed{Eq/E_b = \frac{NP\phi Z}{60A}}$$

Q: A 4 pole DC machine has 60 slots and 8 conductors per slot. The total flux per pole is 20mWb. For a relative speed of 1500 rpm between field flux and armature winding, calculate the generated armature voltage if the armature winding is connected as a) lap connected b) wave connected.

$$P=4, N=1500 \text{ rpm}, \phi = 20 \text{ mWb}, Z = 60 \times 8 = 480$$

$$E = \frac{NP\phi Z}{60A}$$

(a) lap connected : $A = P$

$$\Rightarrow E = \frac{NP\phi Z}{60P} = \frac{1500 \times 20 \times 10^{-8} \times 480}{60} = \underline{\underline{240V}}$$

(b) Wave connected, $A = 2$

$$\Rightarrow E = \frac{N\phi Z}{60A} = 2 \times 240 = \underline{\underline{480V}}$$

Determination of Torque of a machine

Torque produced by the armature is depending on back emf or force developed by the armature and radius of the armature.

Work done by the force which have been developed in the armature is $F \cdot 2\pi r = W$

Finally the power developed by the armature is

$$P = W/t = F \cdot 2\pi r / t/n = nF \cdot 2\pi r$$

Workdone \rightarrow time taken by armature to complete one revolution.

$$T = F \cdot r$$

$$P = T \cdot 2\pi n = T \times 2\pi N / 60$$

$$T = P / 2\pi n$$

$$P = WT$$

Q: A 6 pole DC machine has 300 conductors and each conductor is capable of carrying 80A without excessive temperature rise. The total flux per pole is 15mwb and the machine is driven at speed of 1800 rpm. calculate the total current, emf, power developed in the armature and electromagnetic torque, if the armature winding is a) wave connected b) lap connected.

(b) Wave connected, $A = 2$

$$\Rightarrow E = \frac{N\phi Z}{60A} = 2 \times 240 = \underline{\underline{480V}}$$

Determination of Torque of a machine

Torque produced by the armature is depending on back emf or force developed by the armature and radius of the armature.

Work done by the force which have been developed in the armature is $F \cdot 2\pi r = W$

Finally the power developed by the armature is

$$\text{Work done} \quad P = W/t = F \cdot 2\pi r / Vn = nF \cdot 2\pi r$$

time \rightarrow time taken by armature to complete one revolution.

$$T = F \cdot r$$

$$P = T \cdot 2\pi n = T \cdot 2\pi N / 60$$

$$T = P / 2\pi n$$

$$P = WT$$

Q: A 6 pole DC machine has 300 conductors and each conductor is capable of carrying 80 A without excessive temperature rise. The total flux per pole is 15 mwb and the machine is driven at speed of 1800 rpm. Calculate the total current, emf, power developed in the armature and electromagnetic torque, if the armature winding is a) wave connected b) lap connected.

a) Wave connection: $A = 2$

$$I_a, \text{total current} = 2 \times 80 = \underline{\underline{160A}}$$

$$E_g = \frac{NP\phi Z}{60A} = \frac{1800 \times 8 \times 15 \times 10^{-3} \times 3\phi}{60 \times 2} = \underline{\underline{405V}}$$

$$P = E_g \times I_a = 405 \times 160 = 64.8 \text{ KW}$$

$$T = \frac{E_g I_a}{2\pi N/60} = \underline{\underline{343.77 \text{ Nm}}}$$

b) Lap connected, $A = 6$

$$I_a = 6 \times 80 = \underline{\underline{480A}}$$

$$E_g = \frac{NP\phi Z}{60A} = \frac{1800 \times 8 \times 15 \times 10^{-3} \times 3\phi}{60 \times 6} = \underline{\underline{135V}}$$

$$P = E_g \times I_a = 135 \times 480 = \underline{\underline{64.8 \text{ KW}}}$$

$$T = \frac{E_g I_a}{2\pi N/60} = \underline{\underline{343.77 \text{ Nm}}}$$

Types of DC machines

These are categorized into two parts:


i) self excited DC machines

ii) separately excited DC machines


If the armature & field windings both are connected with the same source - self excited DC machine

If these windings are connected with separate source - separately excited DC machines.

DC machines

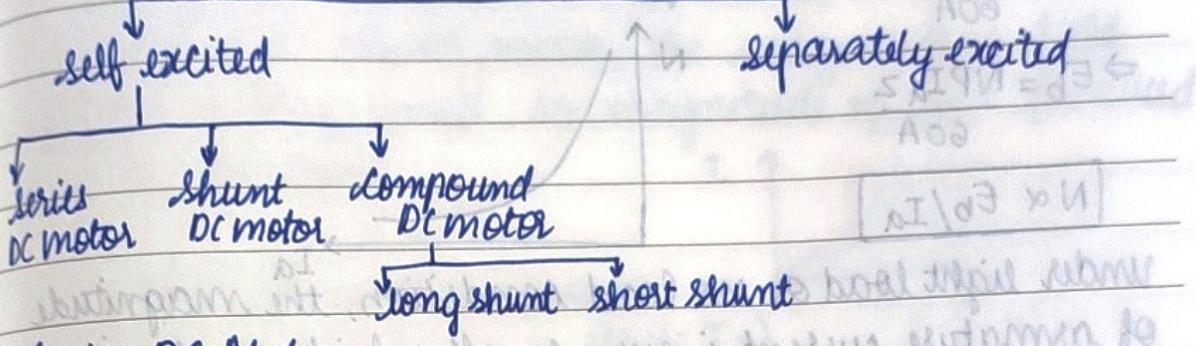


Series DC Motor

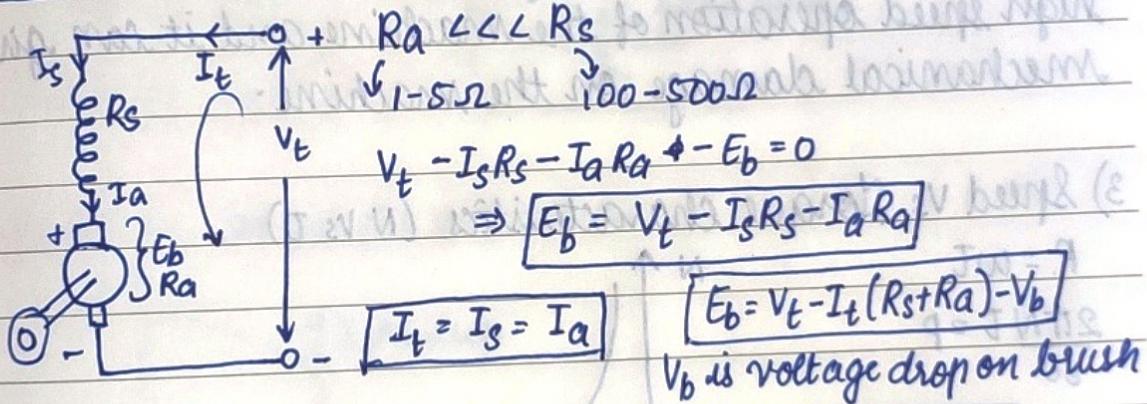

Characteristics of DC series motor:

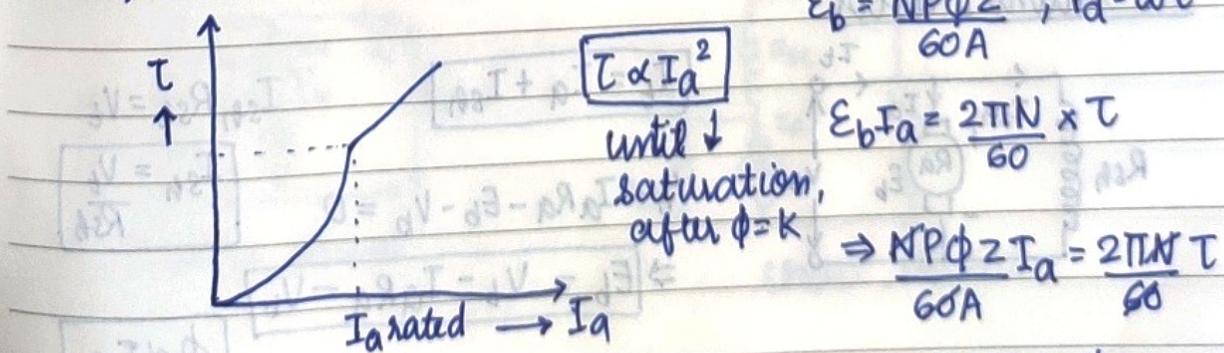i) Torque Vs Armature current characteristics (T vs I_a)



As flux is proportional to I_a because, $\Rightarrow T \propto \phi I_a$
both armature & field windings are connected in series

2) Speed Vs Armature current (N Vs I_a)

$E_b = \frac{NP\phi A Z}{60A}$, In case of series DC motor, $\phi \propto I_a$

$$\Rightarrow E_b = \frac{NPI_a Z}{60A}$$

$$N \propto E_b / I_a$$




under light load or no load condition, the magnitude of armature current is very small which results in high speed operation of the machine and it can give mechanical damage on the machine.

3) Speed Vs Torque characteristics (N Vs T)


$$P = wT$$

$$\frac{2\pi N T}{60} = P$$

$$\Rightarrow N \propto P/T$$

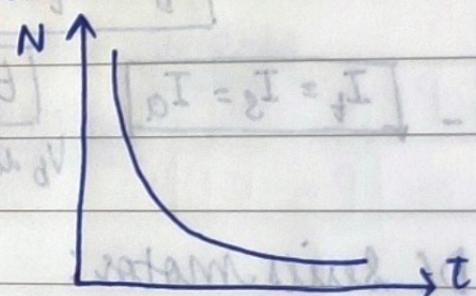

DC shunt motor

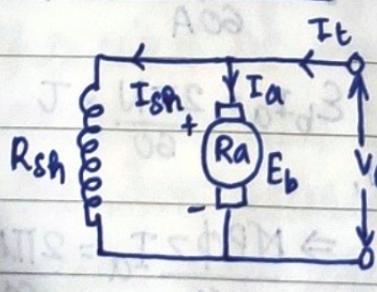

$$I_t = I_a + I_{sh}$$

$$V_t - I_a R_a - E_b - V_b = 0$$

$$\Rightarrow E_b = V_t - I_a R_a - V_b$$

$$I_{sh} R_{sh} = V_t$$


$$I_{sh} = \frac{V_t}{R_{sh}}$$

$$\phi \propto I_{sh}$$

Characteristics of DC shunt motor:

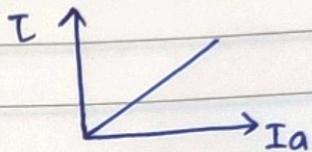1) Torque Vs Armature current (T Vs I_a)


In case of DC shunt motor, the magnitude of field current is very small, so magnitude of flux produced will be constant.




2) Speed Vs Armature current

$$N \propto \frac{E_b}{\Phi} \propto K \text{ by } I_{sh}$$

$$\Rightarrow N \propto V_t - I_a R_a$$

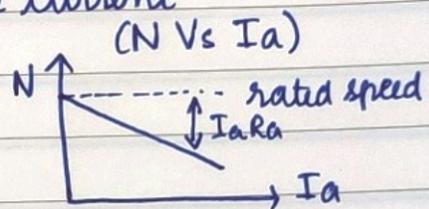

3) Speed Vs Torque (N Vs T)

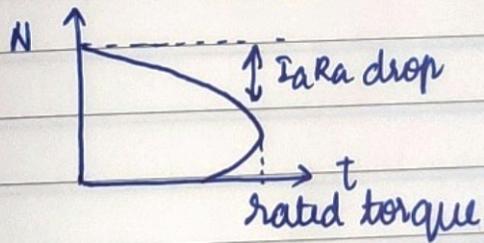

Compound DC motor:

