
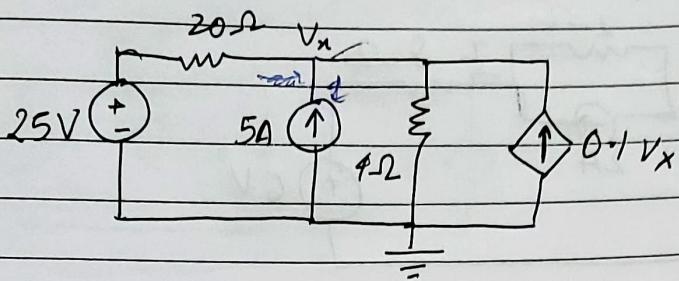


Using superposition theorem, find V_x

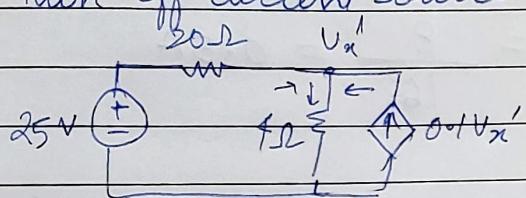

Turn off current source




KCL

$$\frac{V_x' - 25}{20} + \frac{-V_x'}{10} + \frac{V_x'}{4} = 0$$

$$25 = 4V_x'$$

$$V_x' = 6.25 \text{ V}$$

Turn off voltage source


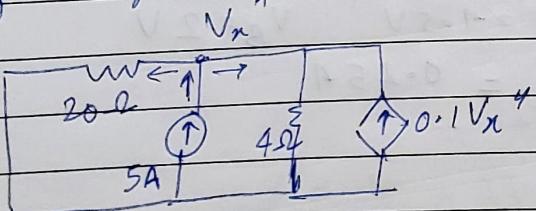


$$\text{KCL}, \quad \frac{V_x \cancel{-25}}{20} + \frac{V_x}{4} = 5 + 0.1V_x''$$


$$V_x'' = 25$$

$$V_x = V_x' + V_x'' = 31.25 \text{ V}$$

Using superposition, find I

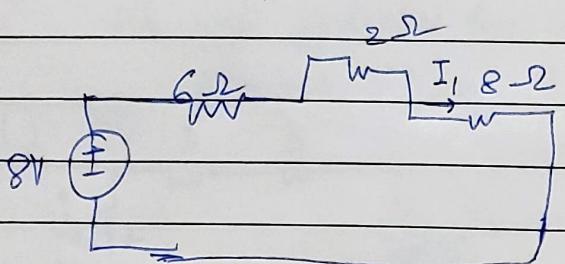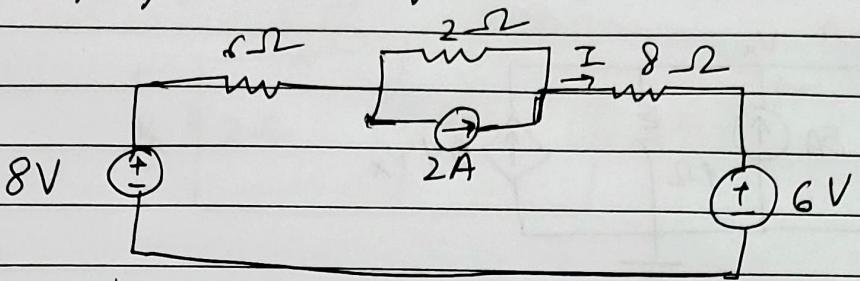

$$I_1 = \frac{8}{16} = 0.5 \text{ A}$$

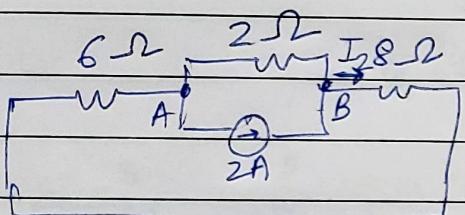

$$\begin{aligned} \text{KCL at } A \\ -\frac{V_A}{6} &= \frac{V_A - V_B}{2} + 2 \end{aligned}$$

$$-4V_A + 3V_B = 12$$


KCL at B

$$\frac{V_A - V_B}{2} + 2 = \frac{V_B}{8}$$

$$4V_A - 5V_B = -16$$

$$V_A = -1.5 \text{ V} \quad V_B = 2 \text{ V}$$

$$I_2 = 0.25 \text{ A}$$


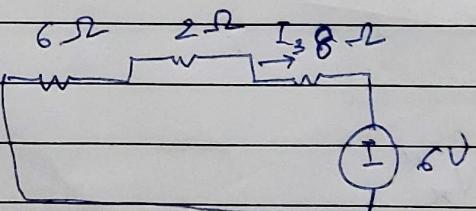


$$I_3 = -\frac{6}{16} = -0.375$$

$$I = I_1 + I_2 + I_3$$

$$= 0.375 \text{ A}$$


Using superposition, find i_x

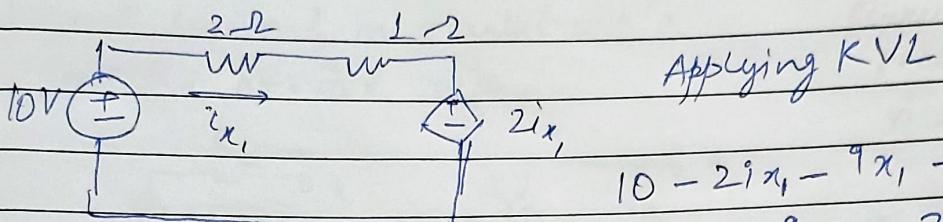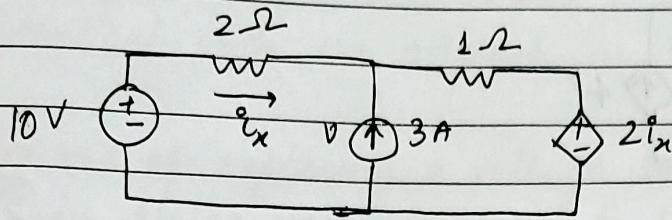

$$\text{Applying KVL}$$

$$10 - 2i_x - 3x_1 - 2i_x = 0$$

$$3x_1 = 24$$

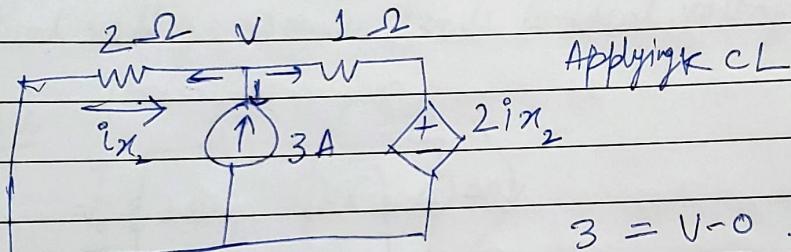

$$\text{Applying KCL}$$

$$3 = \frac{V-0}{2} + \frac{V-2i_x}{1}$$

~~$$i_x = \frac{0-V}{2} = -\frac{V}{2}$$~~

$$2i_x = -V$$

$$3 = \frac{V}{2} + 2V$$

$$V = 6/5$$

$$i_{x_2} = -0.6 A$$


$$i_x = i_{x_1} + i_{x_2} = 2 - 0.6 = 1.4 A$$

Source Transformation


An equivalent circuit is one whose V-I characteristics are identical with the original circuit.

Process of replacing a voltage source

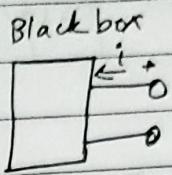V_s in series with a resistor R by a current source i_s in parallel with a resistor R , or vice versa.





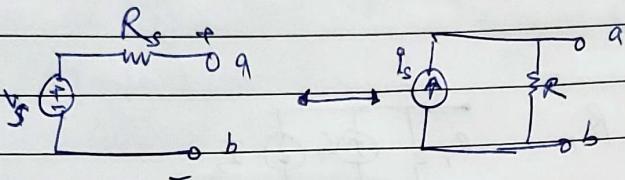
Current entering +ve terminal
passive sign convention
 $v_i = \text{power absorbed}$.




$$V_s = i_s R \text{ or } i_s = \frac{V_s}{R}$$

As R_s tends to zero

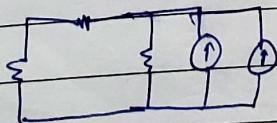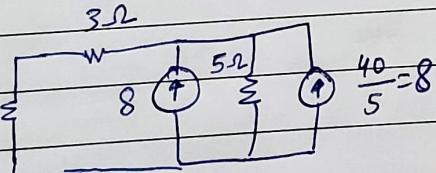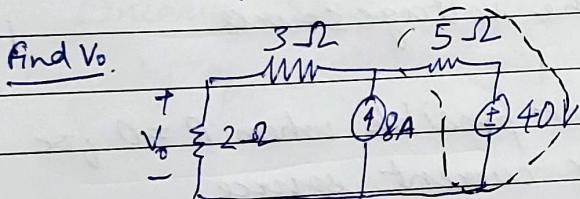Real voltage source tends to ideal voltage source




$$(I_1 + I_2) = 8 + 8 = 16$$

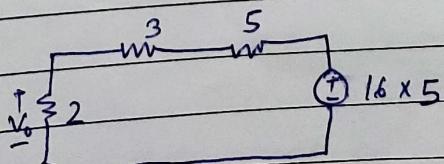

$$\text{Voltage divider} = \frac{V_o}{V_s} = \frac{2}{2+3+5} \times 8$$

Example

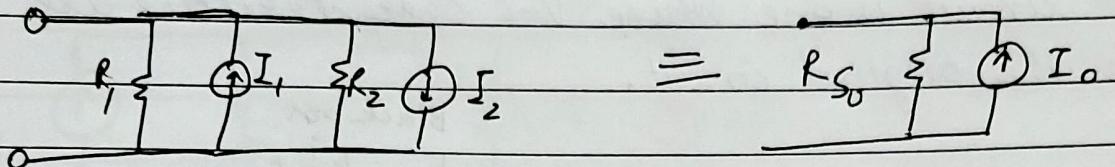


$$I_0 = I_1 - I_2$$

$$R_{S0} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\lim_{R_2 \rightarrow 0} \frac{R_1 R_2}{R_1 + R_2} = 0$$
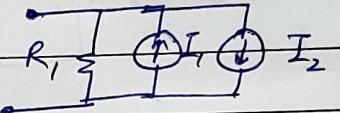
$$\lim_{R_2 \rightarrow \infty} \frac{R_1 R_2}{R_1 + R_2} = R_1$$





- The arrow of the current source is directed toward the positive terminal of the voltage source
- The source transformation is not possible when $R=0$ for voltage source and $R=\infty$ for current source.

Thevenin's Theorem

- A linear two-terminal circuit can be replaced by an equivalent circuit consisting of a voltage source V_{Th} in series with a resistor R_{Th} .

$-V_{Th}$: open-circuit voltage at the terminals.

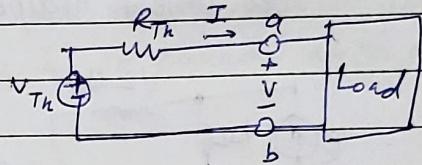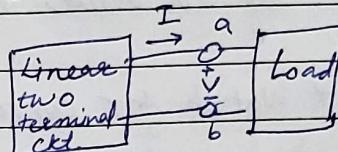$-R_{Th}$: input or equivalent resistance at the terminals when the independent sources are turned off




Linearity Property

- Property of an element describing a linear relationship between cause and effect

- Homogeneity (scaling) property.

$$v = f(i) \rightarrow k^* v = f(k^* i)$$

$$v - iR \rightarrow kv = k iR$$

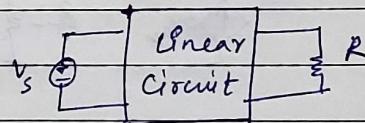

- Superposition (additivity) property

$$\star v_1 = f(i_1) \text{ and } v_2 = f(i_2) \rightarrow v = f(i_1 + i_2) = v_1 + v_2$$



$$v_1 = i_1 R \text{ and } v_2 = i_2 R \rightarrow v = (i_1 + i_2) R = v_1 + v_2$$

- A circuit element (or device) is said to possess the property of linearity when it follows the principle of Homogeneity (scaling) and superposition (additivity).
- A linear circuit is one whose output is linearly related (or directly proportional) to its input.

Norton's Theorem

- A linear two-terminal circuit can be replaced by an equivalent circuit of a current source I_N in parallel with a resistor R_N .

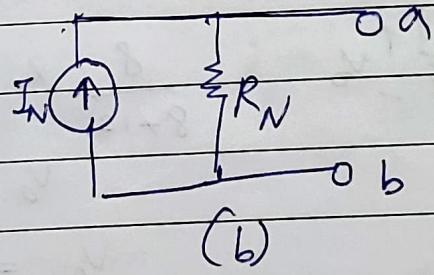
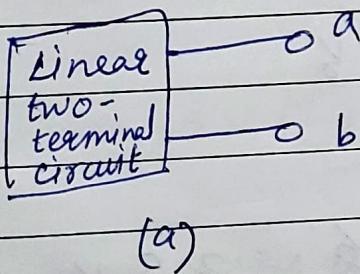
- I_N : short circuit current through the terminals
- R_N : input or equivalent resistance at the terminals when the independent sources are turned off



The Thevenin's and Norton equivalents are related by source transformation


finding R_N & R_{Th} with dependant sources

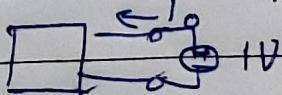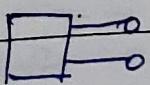Turn off independent source and leave dependant source as it is. Attach voltage of 1V and find i_o in that branch



$$\frac{R_N}{R_{Th}} = \frac{1}{i_o}$$

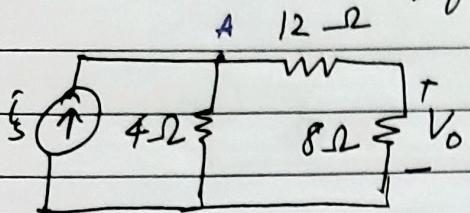For this circuit, find V_o when $\zeta_s = 30$ and $i_s = 45A$



KCL at A

$$i_s = \frac{V_A}{4} + \frac{V_A}{20}$$

$$V_A = \frac{20 \times 18}{6}$$


$$V_o = \frac{8}{8+12} \times V_A$$

$$= \frac{8}{20} \times \frac{20}{6} i_s$$

$$V_o = \frac{4}{3} \times 18$$

$$\zeta_s = 30 \quad V_o = 40 \quad i_s = 45, \quad V_o = 60$$

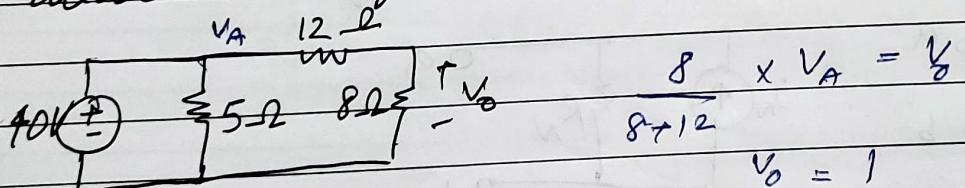Assume that $V_o = 1V$ and use linearity to calculate the actual value of V_o in the circuit



$$\frac{8}{8+12} \times V_A = 1$$


$$V_A = 1$$

$$V_o = 20/8 = 2.5V$$

But in reality $V_A = 40$


$$V_o = 1 \times \frac{40}{2.5} = 16V$$

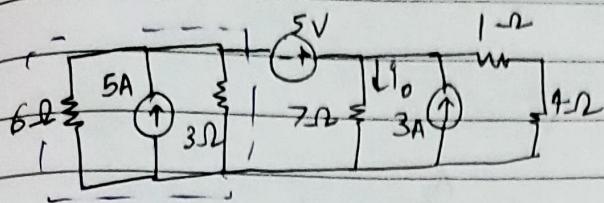Find i_o in the circuit shown using source transformation




$$6//3 \quad \frac{6 \times 3}{6+3} = 2\Omega$$

$$V = IR = 10V$$

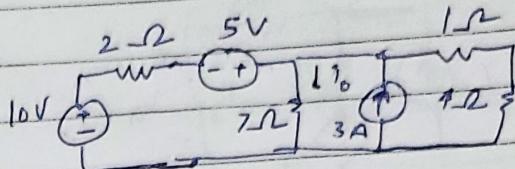


$$I = \frac{V}{R} = \frac{10}{2} = 5A$$

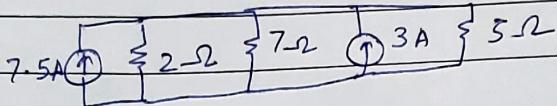


$$I = 7.5 + 3$$
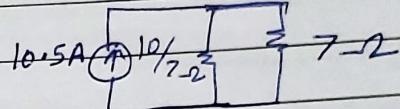
$$R = \frac{2 \times 5}{2+7} = \frac{10}{7}\Omega$$




$$V = 10.5 \times \frac{10}{7} = 15V$$

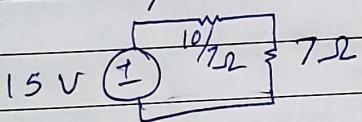


$$i_o = \frac{15}{\frac{10}{7} + 7} = 1.078A$$

Q. Find i_x using source transformation

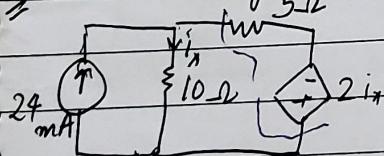
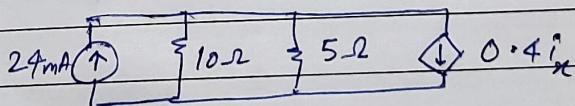
$$R = 5\Omega \quad i_x = \frac{2i_x}{5} = 0.4i_x$$





$$\frac{24}{0.4i_x} \quad V = i_x R \\ = (24 - 0.4i_x)5$$

$$= 120 - 2i_x$$

$$120 - 2i_x \quad i_x = \frac{120 - 2i_x}{15}$$

$$i_x = \frac{120mA}{17}$$

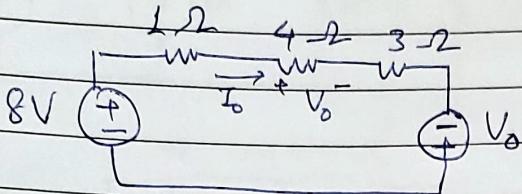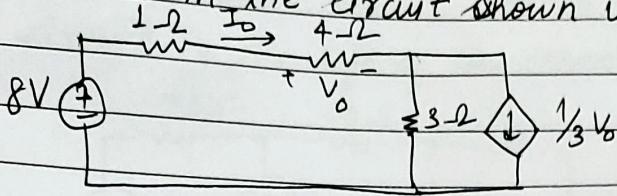Find I_o in the circuit shown using source transformation



$$V = IR$$

$$= \frac{1}{3} V_o \times 3 = V_o$$

$$8 + V_o = I_o \times 8$$




$$V_o = I_o \times 4$$

$$8 + 4I_o = 8I_o$$

$$8 = 4I_o$$




$$I_o = 2 \text{ A}$$

Find V_o using source transformation

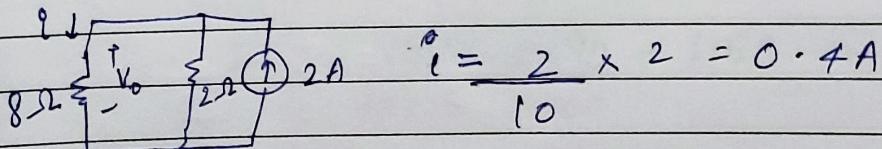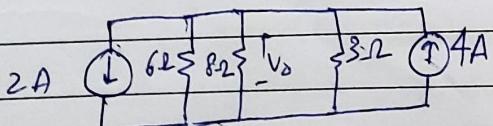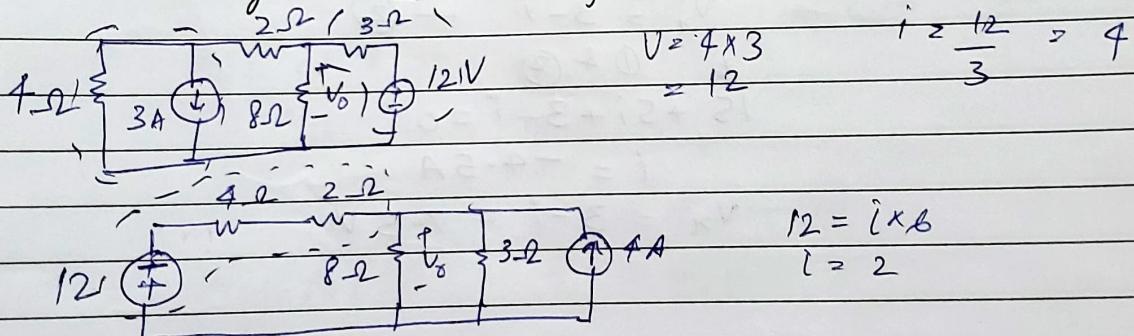

$$V_o = 3 \cdot 2 \text{ V}$$

~~Find~~ i_0

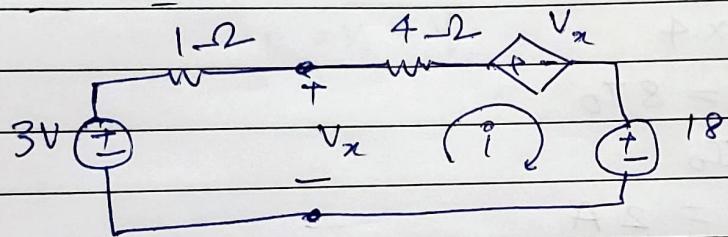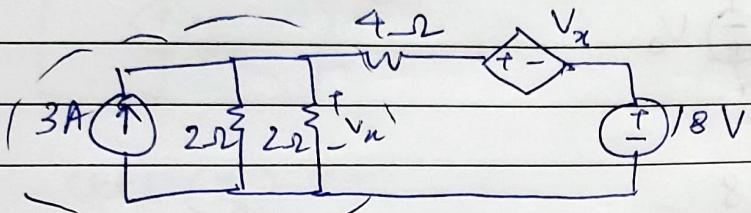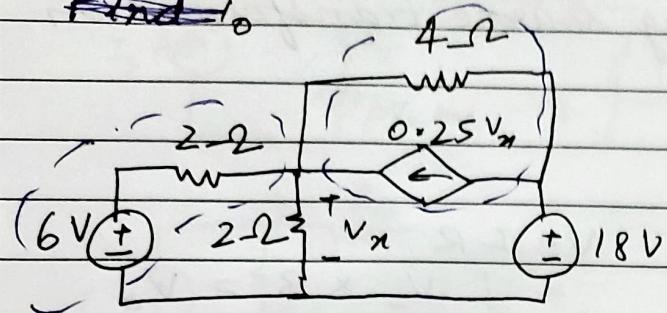

$$3 - 5i - V_x - 18 = 0 \quad \textcircled{1}$$

$$-3 + i + V_x = 0$$

$$V_x = 3 - i \quad \textcircled{2}$$

from $\textcircled{1} \& \textcircled{2}$


$$15 + 5i + 3 - i = 0$$

$$i = -4.5 A$$

$$V_x = 3 - i = 7.5 V$$


M	T	W	T	F	S	S
Page No.:						
Date:						

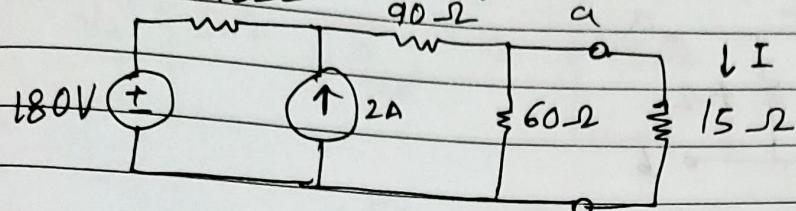For the circuit shown, obtain the Thvenin equivalent of the circuit to the left of the terminals a and b. Then find I.



$$\begin{aligned}
 R_{Th} &= \frac{(90+90)}{60} = 180/60 \\
 &= 3 \Omega
 \end{aligned}$$
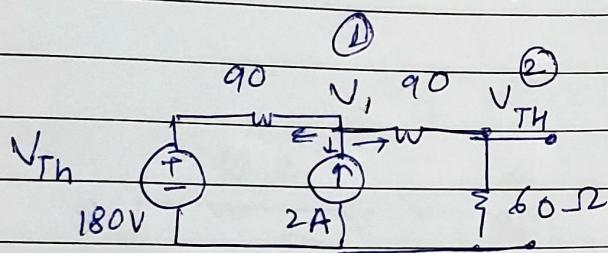
$$R_{Th} = \frac{180 \times 60}{240} = 45 \Omega$$



KCL at Node 1

$$\frac{V_1 - 180}{90} - 2 + V_1 - V_{Th} = 0$$


~~$$2V_1 - V_{Th} - 180 = 0 \quad (1)$$~~

KCL at Node 2

$$\frac{V_{Th} - V_1}{90} + \frac{V_{Th} - 0}{60} = 0$$


$$5V_{Th} - 2V_1 = 0 \quad (2)$$

From (1) & (2) $V_{Th} = 90V$

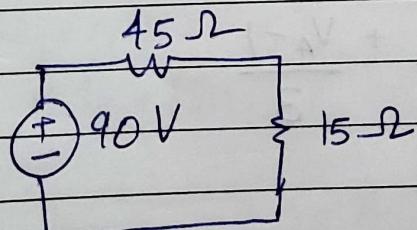

$$I = \frac{90}{45+15} = \frac{90}{60} = 1.5A$$

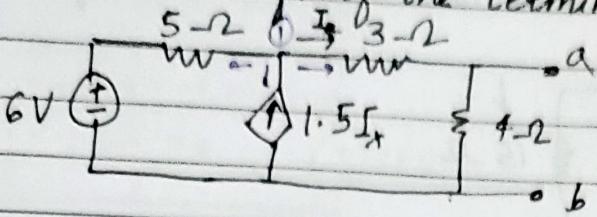For the circuit shown, obtain the Thvenin equivalent of the circuit to the left of the terminals a and b



KCL at ①

$$\frac{V_1 - 6}{5} + -1.5I_x + \frac{V_1 - 0}{3} = 0$$


$$I_x = \frac{V_1}{7}$$

$$\frac{V_1 - 6}{5} - \frac{1.5V_1}{7} + \frac{V_1}{7} = 0$$

$$84 = 9V_1$$

$$V_1 = 84/9$$
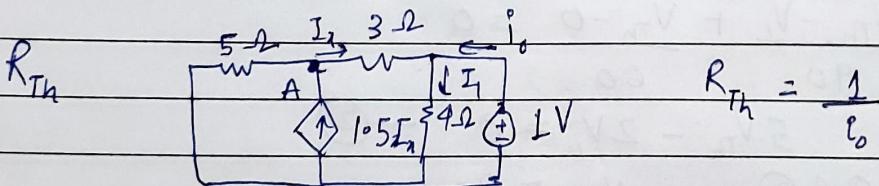
$$V_{Th} = \frac{84}{9} \times \frac{4}{7} = \frac{48}{9} = 5.333V$$



KCL at A

$$1.5I_x = \frac{V_A}{5} + \frac{V_A - 1}{3}$$

$$I_x = \frac{V_A - 1}{3}$$

$$1.5 \times \frac{V_A - 1}{3} = \frac{V_A}{5} + \frac{V_A - 1}{3}$$


$$V_A = -5V$$

$$I_o + I_x = I_1$$

$$I_o = I_1 - I_x$$

$$= \frac{1}{4} - \frac{-5-1}{3} = 2.25A$$

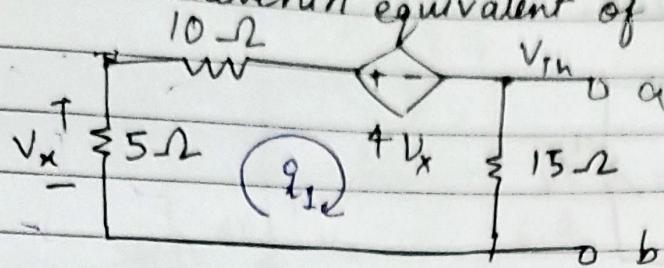Obtain Thvenin equivalent of the circuit.



$$-5i_1 - 10i_1 - 4V_x - 15i_1 = 0$$

$$-30i_1 = 4V_x$$


$$V_x = -i_1 \times 5$$

$$-30i_1 = -20i_1$$

$$10i_1 = 0$$

$$i_1 = 0$$

$$V_{Th} = 15i_1 = 0$$

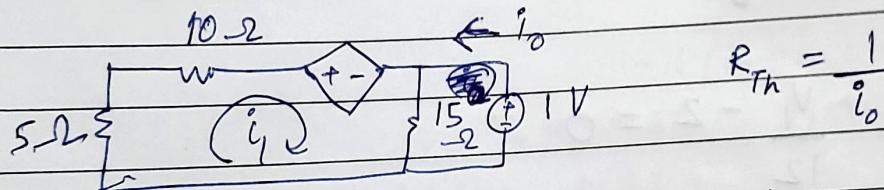

$$\text{Mesh 1} \quad V_x - 10i_1 - 4V_x - 15(i_0 + i_1) = 0$$

$$3V_x + 25i_1 + 15i_0 = 0$$

$$-15i_1 + 25i_1 + 15i_0 = 0$$

$$15i_0 + 10i_1 = 0 \quad -\textcircled{1}$$

Mesh 2


$$-15(i_0 + i_1) + 1 = 0$$

$$15i_0 + 15i_1 = 1 \quad -\textcircled{2}$$


$$i_0 = -2/15 \text{ A}$$

$$R = \frac{1}{-2/15} = -7.5 \Omega$$

Q Obtain Thevenin equivalent.

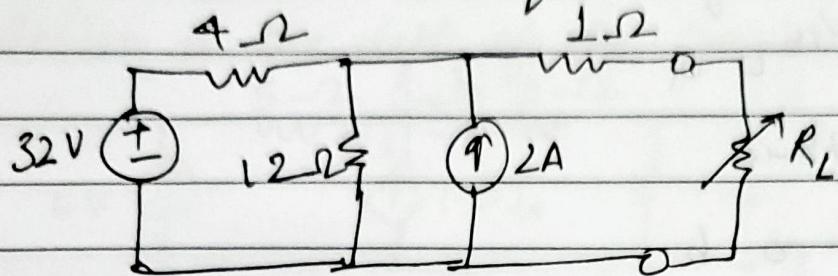
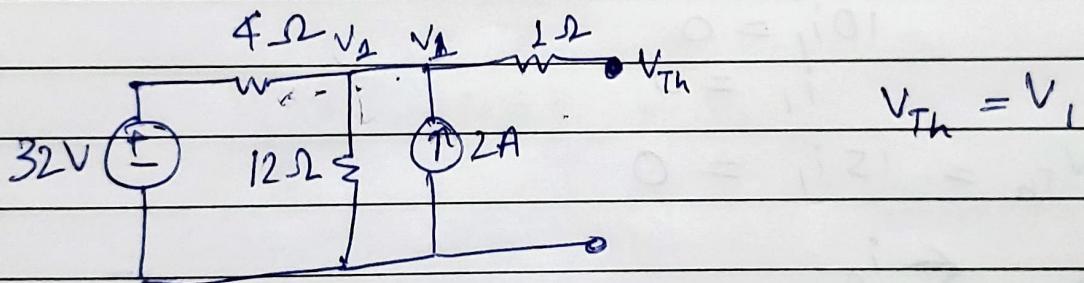
$$R_{Th} = \frac{(4 \parallel 12) + 1}{3 + 1} = 4 \Omega$$



$$\frac{V_1 - 32}{4} + \frac{V_1}{12} - 2 = 0$$



$$3V_1 - 96 + V_1 - 24 = 0$$

$$4V_1 = 120$$

$$V_1 = 30 \text{ V}$$

$$V_{Th} = 30 \text{ V}$$

Obtain Thvenin equivalent

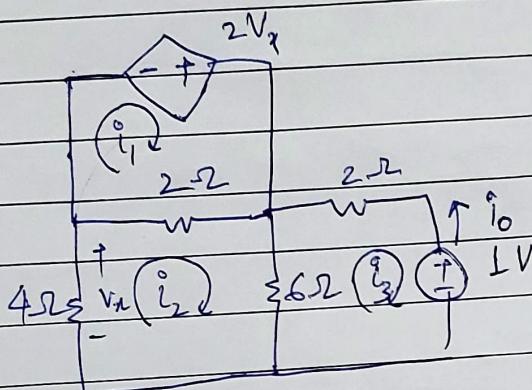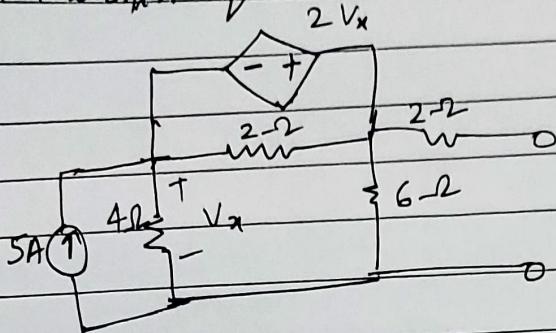

Mesh 1

$$2V_x - 2(i_1 - i_2) = 0$$

$$V_x = i_1 - i_2 \quad \text{---(1)}$$

Mesh 2

$$-4i_2 - 2(i_2 - i_1) - 6(i_2 - i_3) = 0$$

$$\text{---(2)}$$

Mesh 3


$$-6(i_3 - i_2) - 2i_3 = 0 \quad \text{---(3)}$$

$$V_x = -4i_2 = i_1 - i_2 \quad \text{---(4)}$$

Solving. 2, 3 & 4

$$i_3 = -1/6 A \quad i_0 = -i_3$$

$$R_{Th} = \frac{1}{-i_3} = 6\Omega$$

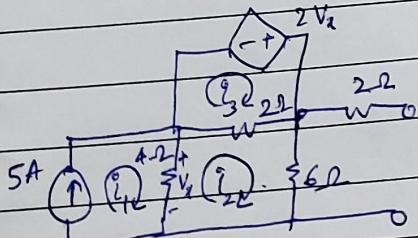

$$i_1 = 5$$

$$2V_x - 2(i_3 - i_2) = 0$$

$$V_x = i_3 - i_2$$

$$-4(i_2 - i_1) - 2(i_2 - i_3) - 6i_2 = 0$$



$$12i_2 - 4i_1 - 2i_3 = 0$$

$$V_x = -4(i_2 - i_1)$$

$$i_2 = 10/3$$


$$V_{Th} = 6i_2 = 20V$$

Obtain Norton equivalent

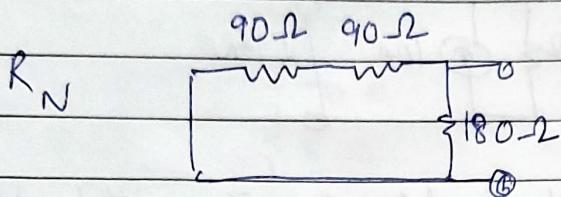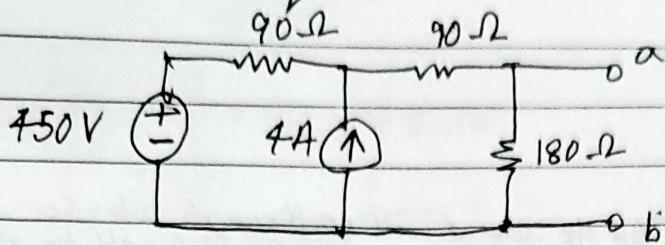

$$R_N = (90 + 90) // 180$$

$$= 90 \Omega$$

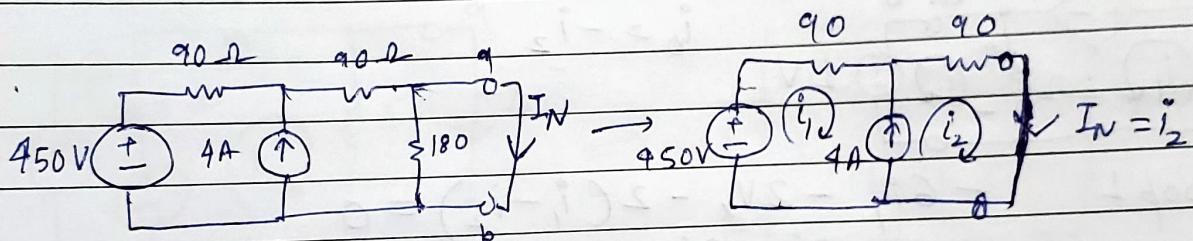

KVL in Supermesh.

$$450 - 90i_1 - 90i_2 = 0$$

$$i_1 + i_2 = 5 \quad -\textcircled{1}$$



$$i_2 - i_1 = 4 \quad -\textcircled{2}$$

$$2i_2 = 9$$

$$i_2 = 4.5 \text{ A}$$


$$I_N = 4.5 \text{ A}$$

Obtain Norton equivalent

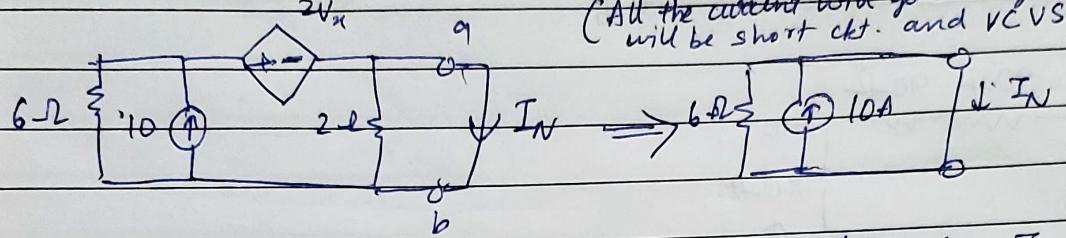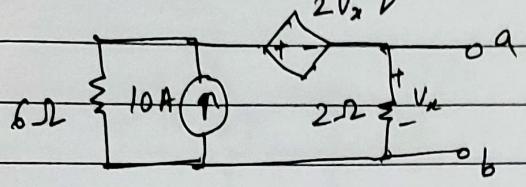

(All the current will go through ab so 2Ω will be short ckt. and VCVS will be removed)

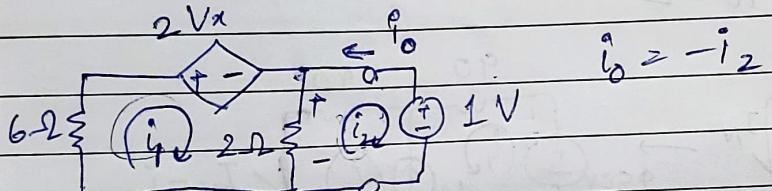Similarly 6Ω will be short ckt. so I_N will be 10A
 $I_N = 10A$



$$\text{Loop L} \quad -6i_1 - 2V_x - 2(i_1 - i_2) = 0 \\ -8i_1 + 2i_2 = 2V_x \quad \text{---(1)}$$

$$\text{Loop 2} \quad -2(i_2 - i_1) = 1 \quad \text{---(2)}$$

$$\text{Also} \quad -2(i_2 - i_1) = V_x \quad \text{---(3)}$$

$$N_x = 1.$$

$$-8i_1 + 2i_2 = 2$$



$$2i_1 - 2i_2 = 1$$

$$i_1 = -\frac{1}{2} A$$


$$i_2 = -1 A$$

$$i_0 = 1 A$$

Obtain Thvenin equivalent.

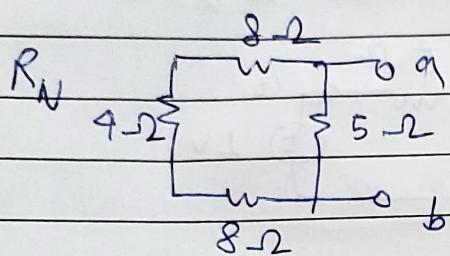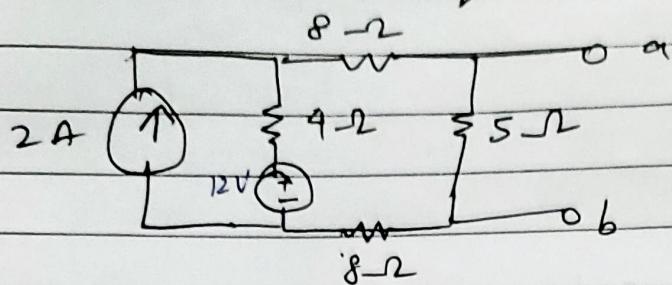
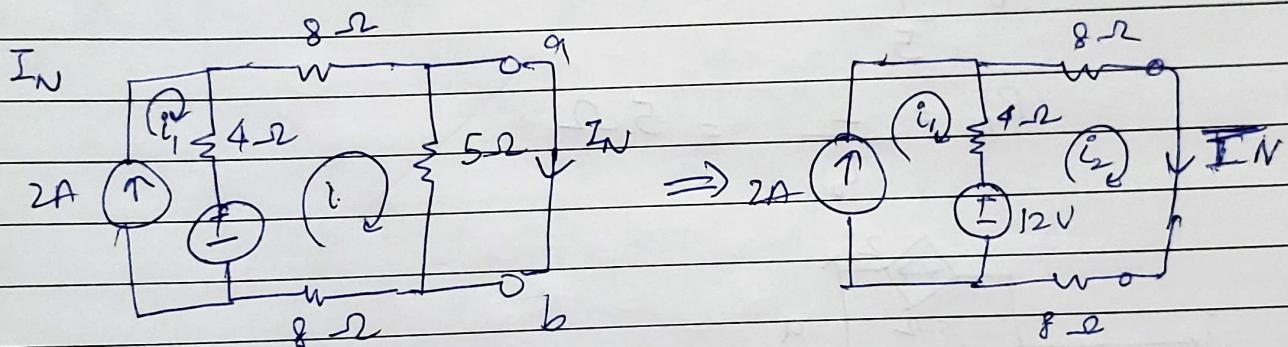
$$R_N = \frac{(8+8+4)}{5} = \frac{20 \times 5}{25} = 4\Omega$$



$$i_1 = 2A$$

KVL in loop 2


$$12 - 4(i_2 - 2) - 8i_2 - 8i_2 = 0$$

$$20i_2 = 20$$


$$i_2 = 1A$$

$$I_N = 1A$$

Q) Obtain Norton equivalent.

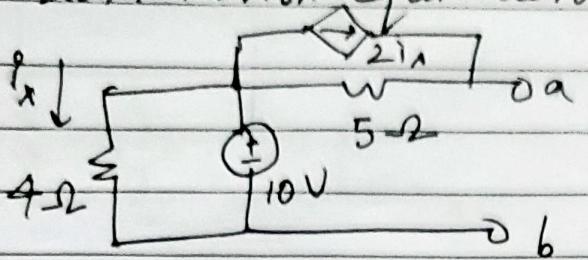


4Ω is short ckt'd. so $i_x = 0$

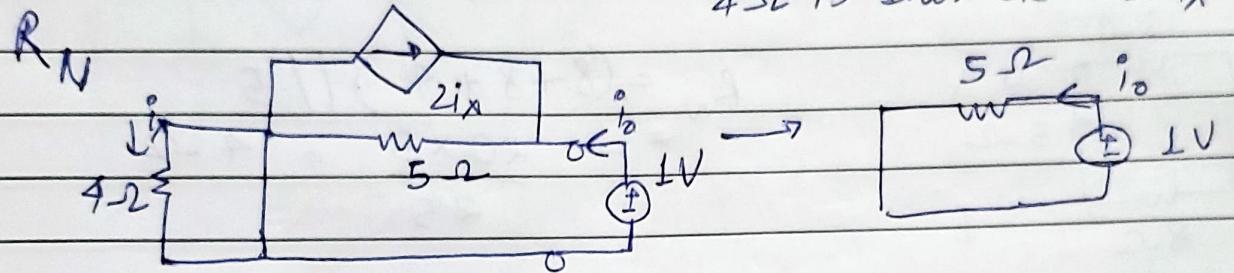

$$i_o = \frac{1}{5}$$

$$R_N = \frac{1}{i_o} = 5\Omega$$

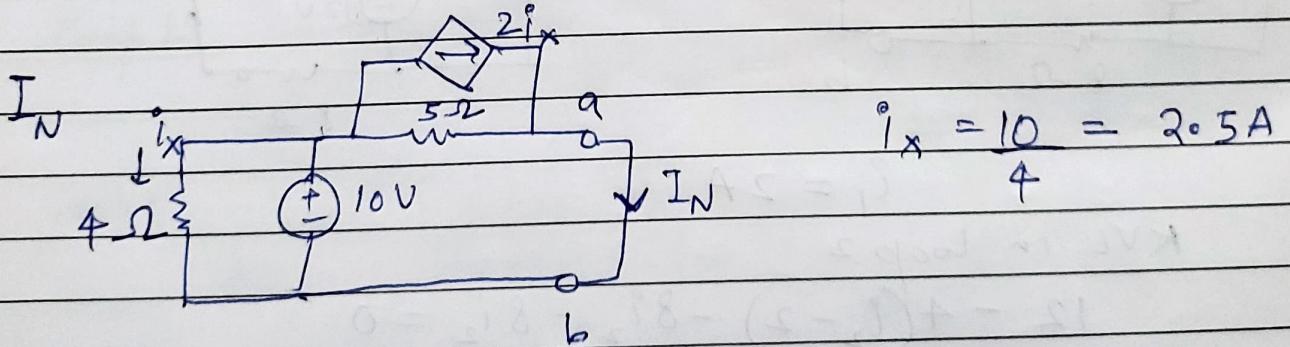

$$i_x = \frac{10}{4} = 2.5A$$

$$I_N = \frac{10 + 2i_x}{5}$$


$$= \frac{10}{5} + 2 \times 2.5$$

$$= 7A$$

Maximum Power transfer


- If the entire circuit is replaced by its Thvenin equivalent except for the load, the power delivered to the load is:
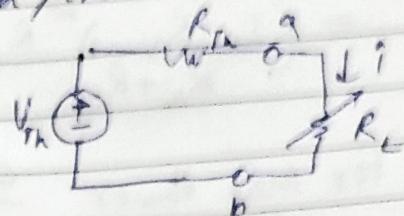
$$P = i^2 R_L = \left[\frac{V_{Th}}{R_{Th} + R_L} \right]^2 R_L$$




- For maximum power dissipated in R_L , P_{max} (for a given R_{Th} and V_{Th})
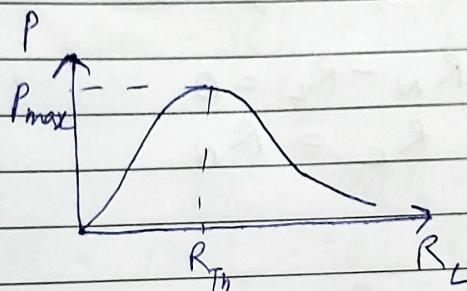
$$R_L = R_{Th} \Rightarrow P_{max} = \frac{V_{Th}^2}{4R_L}$$



Proof of MPT

Thvenin ckt.

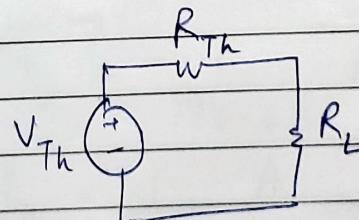

$$P = i^2 R_L$$

$$= \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$


$$\text{for Max Power } \frac{dP}{dR_L} = 0$$

$$\frac{dP}{dR_L} = V_{Th}^2 \left[\frac{(R_{Th} + R_L)^2 - 2R_L(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right]$$

$$= V_{Th}^2 \left[-\frac{R_{Th} - R_L}{(R_{Th} + R_L)^3} \right] = 0$$

$$\Rightarrow R_{Th} = R_L$$

Norton Ckt.

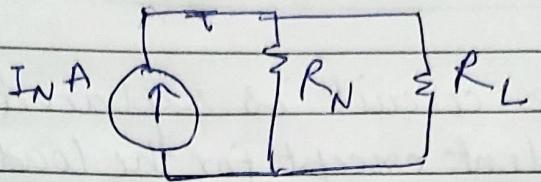

$$P = i^2 R_L$$

$$= \left(\frac{I_N R_N}{R_N + R_L} \right)^2 R_L$$

for Max Power $\frac{dP}{dR_L} = 0$



$$\frac{dP}{dR_L} = I_N^2 R_N^2 \left[\frac{(R_N + R_L)^2 - 2R_L(R_N + R_L)}{(R_N + R_L)^4} \right]$$

$$= I_N^2 R_N^2 \left[\frac{(R_N + R_L) - 2R_L}{(R_N + R_L)^3} \right] = 0$$

$$R_N - R_L = 0$$

$$R_L = R_N$$

Find the value of R_L that will draw maximum power from the rest of the ckt. Find max power.

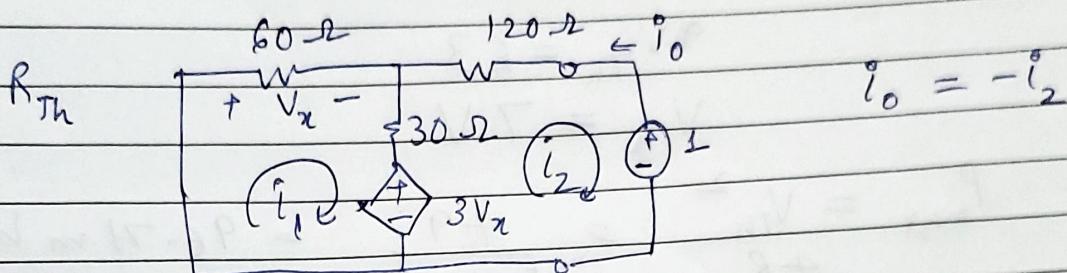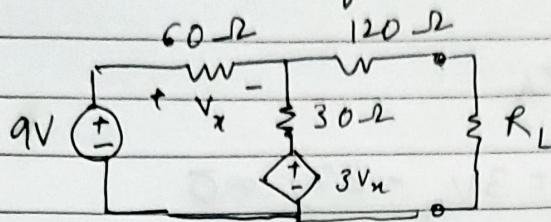

Loop 1

$$-60i_1 - 30(i_1 - i_2) - 3V_x = 0$$

$$V_x = 60i_1$$

$$-60i_1 - 30i_1 + 30i_2 - 180i_1 = 0$$

$$i_2 = 9i_1 \quad \text{--- (1)}$$

Loop 2

$$3V_x - 30(i_2 - i_1) - 120i_2 - 1 = 0$$

$$180i_1 - 30i_2 + 30i_1 - 120i_2 = 1$$


$$210i_1 - 150i_2 = 1$$

using (1)

$$i_2 = -\frac{1}{126.67} \text{ A}$$

$$i_0 = \frac{1}{126.67} \text{ A}$$
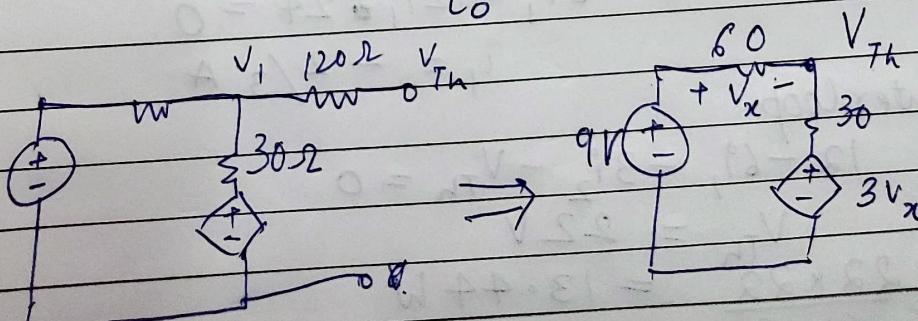
$$R_{Th} = \frac{1}{i_0} = 126.67 \Omega$$



$$\frac{V_{Th} - 9}{60} + \frac{V_{Th} - 3V_2}{30} = 0$$

$$V_2 = 9 - V_{Th}$$


$$V_{Th} - 9 + 2(V_{Th} + 3V_{Th} - 27) = 0$$

$$9V_{Th} = 63$$

$$V_{Th} = 7V$$

$$P_{max} = \frac{V_{Th}^2}{4R_L} = \frac{49}{4 \times 126.67} = 96.71 \text{ mW}$$

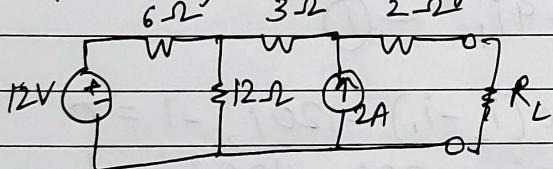Q. Find the value of R_L that will draw maximum power from rest of the circuit. Find max power



$$R_{Th} = \left(\frac{6 \parallel 12}{6+12} \right) + 3 + 2 = \frac{6 \times 12}{18} + 3 + 2 = 4 + 3 + 2 = 9 \Omega$$

$$V_{Th} = 12V$$

$$i_2 = -2A$$

$$\text{Loop 1: } 12 - 6i_1 - 12(i_1 - i_2) = 0$$

$$12 - 6i_1 - 12i_1 + 24 = 0$$

$$i_1 = -\frac{2}{3} A$$

KVL in outer loop

$$12 - 6i_1 - 3i_2 - V_{Th} = 0$$

$$V_{Th} = 22V$$

$$P_{max} = \frac{22 \times 22}{4 \times 9} = 13.44 W$$