

* AC Circuit

Sinusoids and Phasors


Sinusoidal signal is easy to generate and transmit
Through Fourier analysis, any practical periodic signal
can be represented by a sum of sinusoids.

$$v(t) = V_m \sin(\omega t + \phi)$$

ϕ = phase

$$\omega = 2\pi f \quad T = 2\pi/\omega \quad f = 1/T$$

+coswt

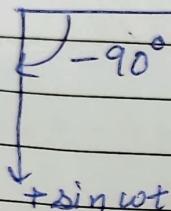

The horizontal axis represents the magnitude of cosine, while the vertical axis (pointing down) denotes the magnitude of sine. Angles are measured +vely clockwise from the horizontal.

Adding 2 sinusoids

$$A \cos \omega t + B \sin \omega t = C \cos(\omega t - \theta)$$

$$C = \sqrt{A^2 + B^2} \quad \theta = \tan^{-1} \frac{B}{A}$$

$v_1 = -10 \cos(\omega t + 50^\circ)$ and $v_2 = 12 \sin(\omega t - 10^\circ)$. Which is leading.

$$v_1 = -10 \cos(\omega t + 50^\circ) = 10 \cos(\omega t + 50 - 180) = 10 \cos(\omega t - 130^\circ)$$

$$v_2 = 12 \sin(\omega t - 10^\circ) = 12 \cos(\omega t - 10 - 90) = 12 \cos(\omega t - 100^\circ)$$

v_2 leads v_1 by 30°

$$\begin{aligned} i_1 &= -4 \sin(377t + 55^\circ) \\ i_2 &= 5 \cos(377t - 65^\circ) \end{aligned}$$

~~$I_{\max}(wt+\theta)$~~
 ~~$\theta = 210^\circ$~~
 $[-\pi, \pi]$

$$I_1(t) = 4 \cos(377t + 145^\circ)$$

$$I_2(t) = 5 \cos(377t - 65^\circ)$$

$$\begin{aligned} i_1 \text{ leads } i_2 \text{ by } & (\theta_1 - \theta_2) \\ & = (145^\circ - (-65^\circ)) = 210^\circ \end{aligned}$$

In this que. If $\theta \in [0, 2\pi]$

$$\theta_1 = 145^\circ$$

$$\theta_2 = -65 + 360 = 295^\circ$$

$$\theta_1 - \theta_2 = -150^\circ$$

i_1 lags i_2 by 150°

Inductive Ckt.

V_L leads I_L by 90°

Capacitive Ckt.

I_C leads V_C by 90°

Phasors

Complex no. $z = x + iy$

$$j = \sqrt{-1}$$

$z = x + iy$ Rectangular form

$z = r\phi$ Polar form

$z = re^{i\phi}$ Exponential form

$$r = \sqrt{x^2 + y^2}$$

$$x = r \cos \phi$$

$$\phi = \tan^{-1} y/x$$

$$y = r \sin \phi$$

$$Z = r/\phi = r(\cos\phi + j\sin\phi)$$

$$\text{Reciprocal } \frac{1}{Z} = \frac{1}{r} \angle -\phi$$

$$\text{Root} \quad \sqrt{Z} = \sqrt{r} \angle \phi/2$$

$$\text{Conjugation } Z^* = r \angle -\phi = r e^{-j\phi}$$

Time domain

$$\begin{cases} V_m \cos(\omega t + \theta) \\ V_m \sin(\omega t + \theta) \end{cases} \Leftrightarrow$$

Phasor domain

$$V_m \angle \theta$$

$$V_m \angle \theta - 90^\circ$$

$$V_m e^{j\theta}$$

$$v(t) = -5 \sin(\omega t + 30^\circ)$$

$$= 5 \cos(\omega t + 30 + 90) = 5 \cos(\omega t + 120) = 5 \angle 120^\circ$$

Passive Element

R

$$Z = R$$

C

$$Z = 1/j\omega C$$

L

$$Z = j\omega L$$

For different freq, impedance will be different.

Dependant Sources

Ex: CCCS

$$i(t) = 5i_x(t) \rightarrow 5I_x$$

$$v(t) \rightarrow v/\theta = \vec{V}_{\text{phasor}}$$

$$\frac{dv(t)}{dt} \rightarrow j\omega \vec{V}_{\text{phasor}} = j\omega V/\theta = \omega V \angle (\theta + \pi/2)$$

$$\int v dt \rightarrow \frac{\vec{V}_{\text{phasor}}}{j\omega} = -\frac{j}{\omega} V/\theta = \frac{V}{\omega} \angle (\theta - \pi/2)$$

Q. Using the phasor approach, determine the current described by the integrodifferential equation.

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

$$4I + \frac{8I}{j\omega} - 3j\omega I = 50 \angle 75^\circ$$

$$\omega = 2$$

$$I(4 - j4 - j6) = 50 \angle 75^\circ$$

$$I = \frac{50 \angle 75^\circ}{4 - j10} = \frac{50 \angle 75}{10.77 \angle -68.2^\circ} = 4.642 \angle 143.2^\circ \text{ A}$$

$$i(t) = 4.642 \cos(2t + 143.2^\circ) \text{ A}$$

Phasor Relationship for Circuit Elements

For Inductor L

$$i = I_m \cos(\omega t + \phi)$$

$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi)$$

$$v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

$$v = \omega L I_m e^{j(\phi + 90^\circ)} = \omega L I_m \angle \phi + 90^\circ$$

$$v = j\omega L i$$

For capacitor C

$$v = V_m \cos(\omega t + \phi)$$

$$i = C \frac{dv}{dt}$$

$$\cdot = -\omega C V_m \sin(\omega t + \phi)$$

$$i = \omega C V_m \cos(\omega t + \phi + 90^\circ)$$


~~$$i = \omega C V_m e^{j(\phi + 90^\circ)} = \omega C V_m \angle \phi + 90^\circ$$~~

$$i = j\omega C v$$

$$v = \frac{i}{j\omega C}$$

Nodal analysis

Find i_x in ckt.

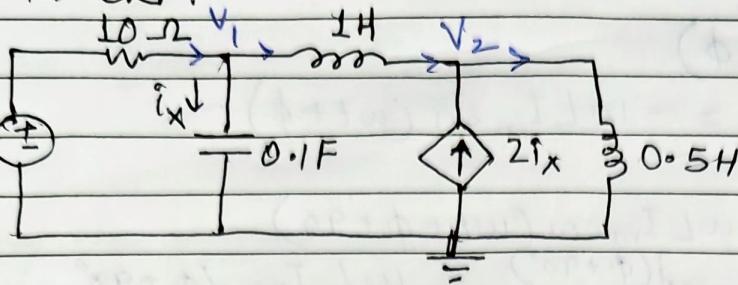

$$20\cos 4t \Rightarrow 20 \angle 0^\circ$$

$$1H = 4j$$

$$0.5H = 2j$$

$$0.1F = -2.5j$$

KCL at node L

$$\frac{20 - V_1}{10} = \frac{V_1}{-2.5j} + \frac{V_1 - V_2}{4j}$$

$$(1 + 1.5j)V_1 + 2.5jV_2 = 20 \quad \text{---(1)}$$

KCL at node 2

$$2I_x + \frac{V_1 - V_2}{4j} = \frac{V_2}{2j}$$

$$I_x = V_1 / -2.5j$$

$$\frac{2V_1}{-2.5j} + \frac{V_1 - V_2}{4j} = \frac{V_2}{2j}$$

$$11V_1 + 15V_2 = 0 \quad \text{---(2)}$$


$$V_1 = 18.97 \angle 18.43^\circ V$$

$$V_2 = 13.91 \angle 198.3^\circ V$$

$$I_x = \frac{V_1}{-2.5j} = \frac{18.97 \angle 18.43^\circ}{2.5 \angle -90^\circ} = 7.59 \angle 108.4^\circ A$$

Mesh Analysis

Determine I_0

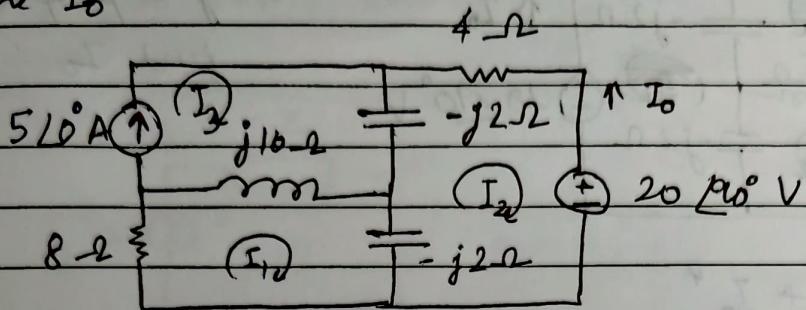

Mesh 1

$$8 + j10 - 8I_1 - 10j(I_1 - I_3) - (-2j)(I_1 - I_2) = 0$$

Mesh 2

$$-4I_2 - 20\angle 90^\circ - (-2j)(I_2 - I_1) - (-2j)(I_2 - I_3) = 0$$

Mesh 3

$$I_3 = 5$$


Solving

$$I_2 = 6.12 \angle -35.22^\circ \text{ A}$$

$$I_0 = -2 = 6.12 \angle 144.78^\circ \text{ A}$$

Superposition


4Ω

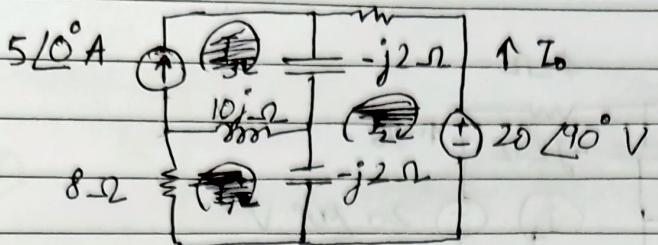

using superposition
find I_o

$$I_o = I_o' + I_o''$$


+2

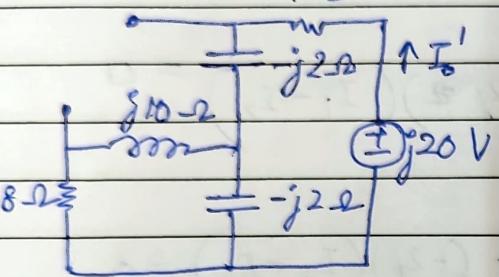

$$Z = \frac{-j^2(8+j10)}{-2j+8+j10} = 8.25-j2.25$$

$$I_o' = \frac{j20}{4-j2+Z} = \frac{j20}{4.25-j4.25}$$

$$I_o' = -2.353 + j2.353$$

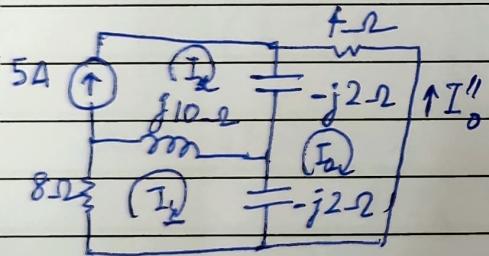

$$\begin{aligned} & \text{Mesh 1} \\ & (8+j8)I_1 - j10I_3 + j2I_2 = 0 \\ & \text{Mesh 2} \\ & (4-j4)I_2 + j2I_1 + j^2I_3 = 0 \end{aligned}$$

Mesh 3

$$I_3 = 5$$


$$I_2 = 2.647 - j1.176$$

$$I_o'' = -I_2 = -2.647 + j1.176$$

$$I_o = I_o' + I_o'' = -5 + j3.529$$

Source Transformation
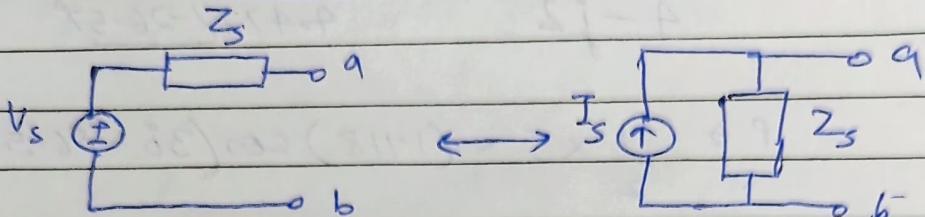
$$V_s = Z_s I_s \Leftrightarrow I_s = \frac{V_s}{Z_s}$$



$$V_s = Z_s I_s$$

$$I_s = \frac{V_s}{Z_s}$$

Thermin and Norton Equivalent Circuits

$$V_{Th} = Z_N I_N, \quad Z_N = Z_N$$

AC Power analysis

$$P(t) = V(t) i(t)$$

$$V(t) = V_m \cos(\omega t + \theta_v)$$

$$i(t) = I_m \cos(\omega t + \theta_i)$$

$$P(t) = V(t) i(t) = V_m I_m \cos(\omega t + \theta_v) \cos(\omega t + \theta_i)$$

$$P(t) = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) + \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i)$$


Average power

$$P = \frac{1}{T} \int_0^T P(t) dt$$

$$P = \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) dt$$

$$+ \frac{1}{T} \int_0^T \frac{1}{2} V_m I_m \cos(2\omega t + \theta_v + \theta_i) dt$$
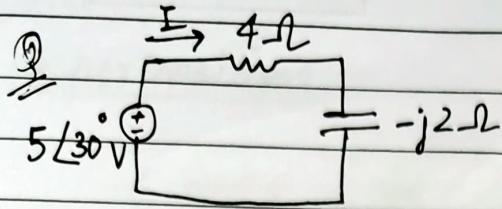
$$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$$



Find Avg. power supplied by source
and avg power absorbed by resistor

$$I = \frac{5\angle 30^\circ}{4-j2} = \frac{5\angle 30^\circ}{4.472\angle -26.57^\circ} = 1.118 \angle 56.57^\circ$$

$$P = \frac{1}{2} \times 5 \times (1.118) \cos(30^\circ - 56.57^\circ) = 2.5 \text{ W}$$

$$I_R = I = 1.118 \angle 56.57^\circ \text{ A}$$


$$V_R = 4I_R = 4 \cdot 4.472 \angle 56.57^\circ \text{ V}$$

$$P = \frac{1}{2} (4.472)(1.118) = 2.5 \text{ W}$$

Maximum Average Power Transfer

$$Z_{Th} = R_{Th} + jX_{Th}$$

$$Z_L = R_L + jX_L$$

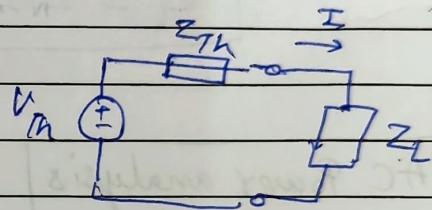

$$I = \frac{V_m}{Z_{Th} + Z_L} = \frac{V_m}{(R_{Th} + jX_{Th}) + (R_L + jX_L)}$$

$$P = \frac{1}{2} |I|^2 R_L = \frac{|V_m|^2 R_L / 2}{(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2}$$

$$\frac{\partial P}{\partial X_L} = - \frac{|V_m|^2 R_L (X_{Th} + X_L)}{[(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial R_L} = \frac{|V_m|^2 [(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2 - 2R_L(R_{Th} + R_L)]}{2 [(R_{Th} + R_L)^2 + (X_{Th} + X_L)^2]^2}$$

$$\frac{\partial P}{\partial X_L} = 0$$

$$X_L = -X_m$$

$$R_L = \sqrt{R_m^2 + (X_m + X_L)^2}$$

$$Z_L = R_L + jX_L = R_m - jX_m$$

$$P_{max} = \frac{|V_m|^2}{8R_m}$$

RMS

Root mean square

$$X_{rms} = \sqrt{\frac{1}{T} \int_0^T x^2 dt}$$

① Square
② mean
③ root

Power Factor

cos of the phase difference between voltage and current

Complex Power

$$S = \frac{1}{2} VI^* \quad (I^* = \text{complex conjugate of current})$$

$$= V_{rms} I_{rms}^*$$

$$S = I_{rms}^* Z$$

$$Z = R + jX$$

$$S = I_{rms}^2 (R + jX) = P + jQ$$

$$S = V_{rms} I_{rms} \angle (\phi_v - \phi_i)$$

$$= V_{rms} I_{rms} \cos(\phi_v - \phi_i) +$$

$$j V_{rms} I_{rms} \sin(\phi_v - \phi_i)$$

$$P = \operatorname{Re}(S) = I_{rms}^2 R$$

$$Q = \operatorname{Im}(S) = I_{rms}^2 X$$

P is average or real power - depends on load's resistance R
 Q is reactive power - depends on load's reactance X


$$P = V_{rms} I_{rms} \cos(\theta_v - \theta_i), \quad Q = V_{rms} I_{rms} \sin(\theta_v - \theta_i)$$

Real power is the actual power dissipated by the load.

Reactive power Q is a measure of energy exchange between source and reactive part of load. Unit of Q is volt-ampere reactive.

- $Q=0$ for resistive loads (unity Power Factor)
- $Q < 0$ for capacitive loads (leading pf)
- $Q > 0$ for inductive loads (lagging pf)

Power Triangle (EE late)

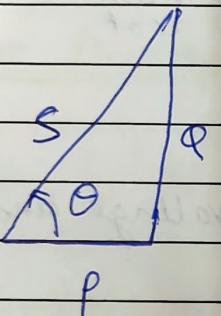


S - Complex power
 Q - Reactive power
 P - Real power
 θ - Power Factor angle

Power Factor Correction

Most inductive domestic & industrial loads are inductive and operate at a low lagging power factor

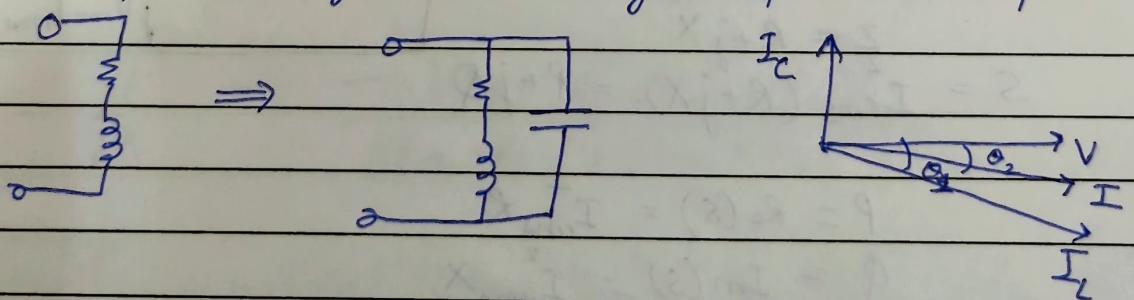PF improved by by installing a capacitor in parallel




Sir's questions

- Appliances which have leading/lagging power factor
 Lagging PF - Transformers, induction motors
 Leading PF - radio ckt's

- Example of 3 phase load in steel industry
 Electric Arc Furnace

Star-Delta

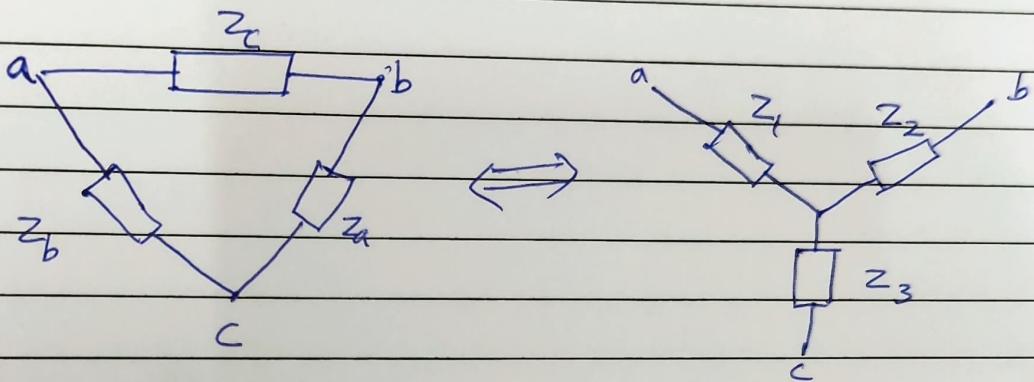

Star to Delta

$$Z_a = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_1}$$

$$Z_b = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_2}$$

$$Z_c = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_3 Z_1}{Z_3}$$

Delta to Star

$$Z_1 = \frac{Z_b Z_c}{Z_a + Z_b + Z_c}$$

$$Z_2 = \frac{Z_c Z_a}{Z_a + Z_b + Z_c}$$

$$Z_3 = \frac{Z_a Z_b}{Z_a + Z_b + Z_c}$$